




Analog Processing

Suresh Devasahayam
Department of Bioengineering
Christian Medical College, Vellore

Lecture - Outline

- Amplifiers
- Frequency filtering
- Filter Characteristics – Gain and Phase
- Phase Distortion in Biological Signals
- Offline Filtering

Measurement schematic

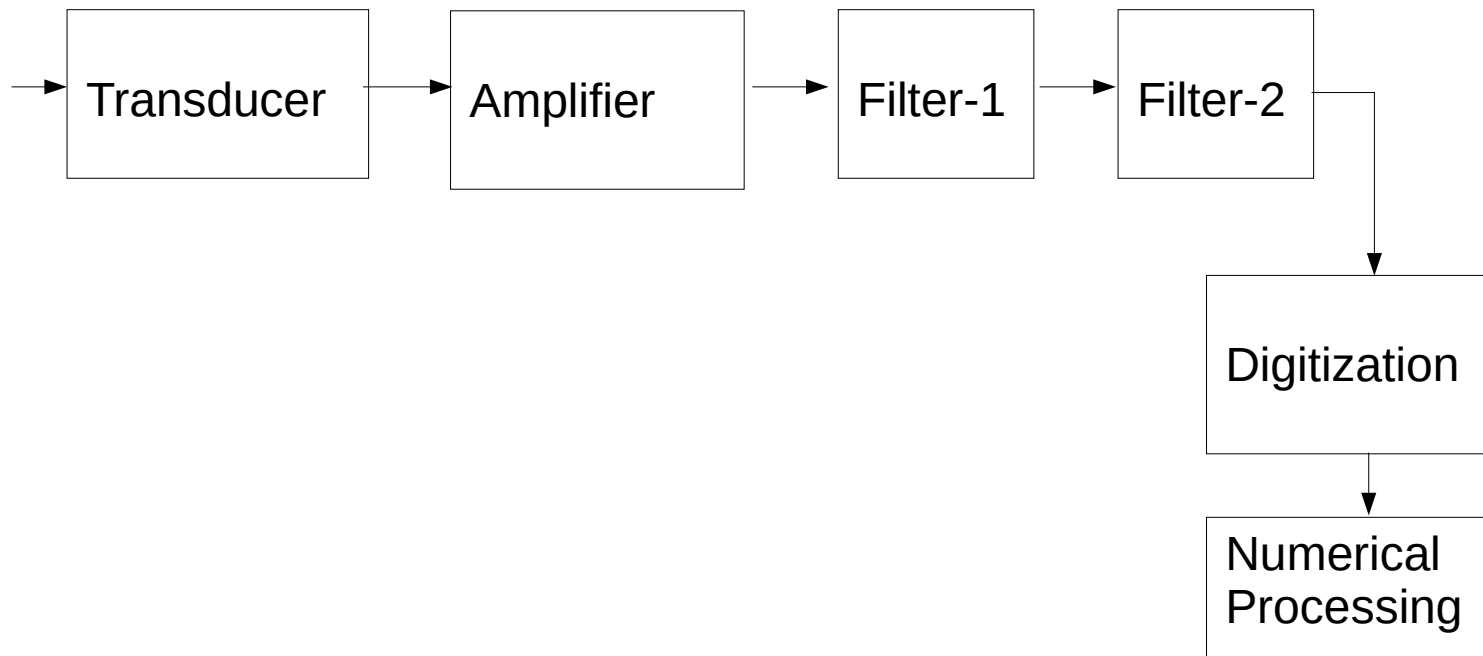



Considerations in Designing Sub-systems (i.e., Transducers, Amplifiers, Filters)

- The subsystem must draw very little power from the preceding subsystem
 - In the case of voltage signals, the subsystem must draw as little current as possible
 - This means the input impedance must be very high
- The subsystem must be capable of delivering as much power as the following or next subsystem requires
 - In the case of voltage signals, the subsystem must be able to deliver as much current as required
 - This means the output impedance must be very small


Thevenin and Norton equivalent for any voltage or current source

- Any voltage or current source can be represented by:
 - A perfect voltage source with a series impedance
 - (Thevenin equivalent)
 - A perfect current source with a shunt impedance
 - (Norton equivalent)

Attenuators and Amplifiers

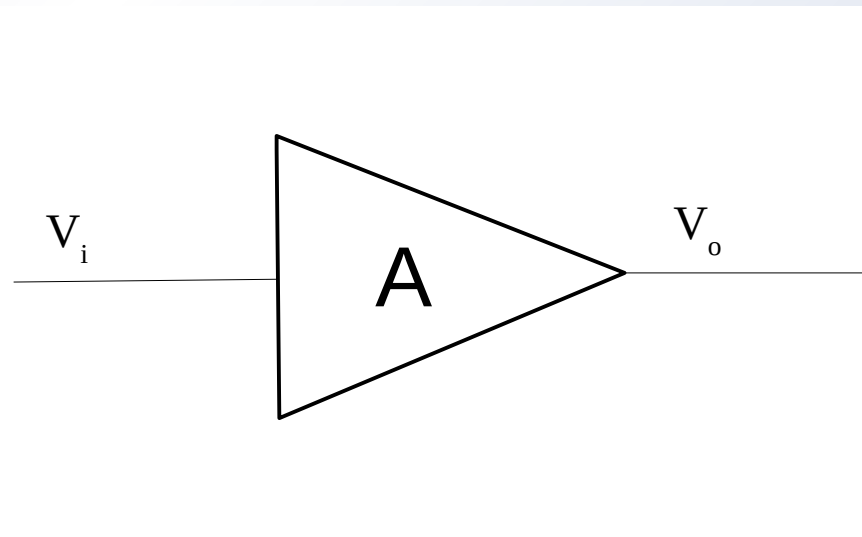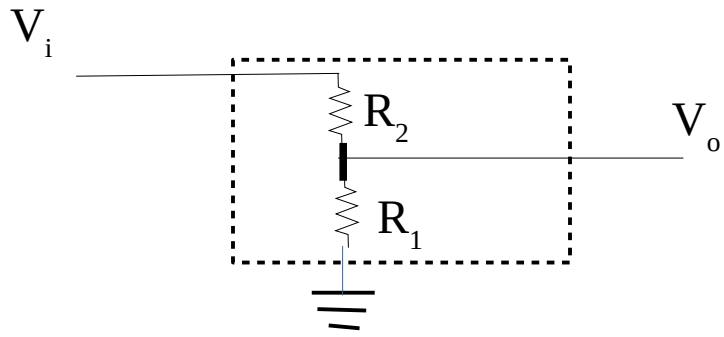


Difference or Differential Amplifier

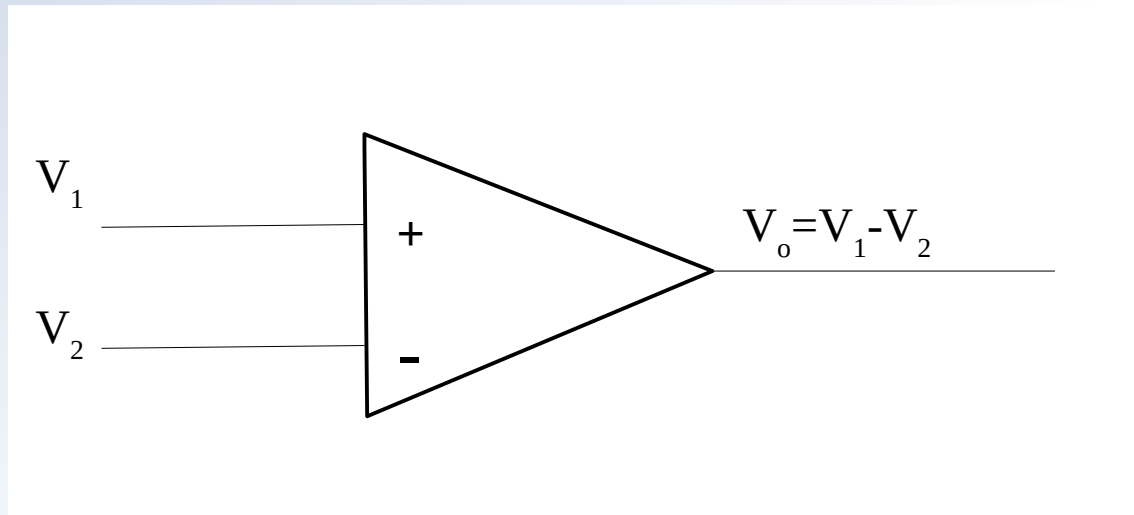

Operational Amplifiers


- Amplifier with differential inputs suitable for feedback circuits
- Very high gain
- Very high input impedance
- Low output impedance

Feedback Control System

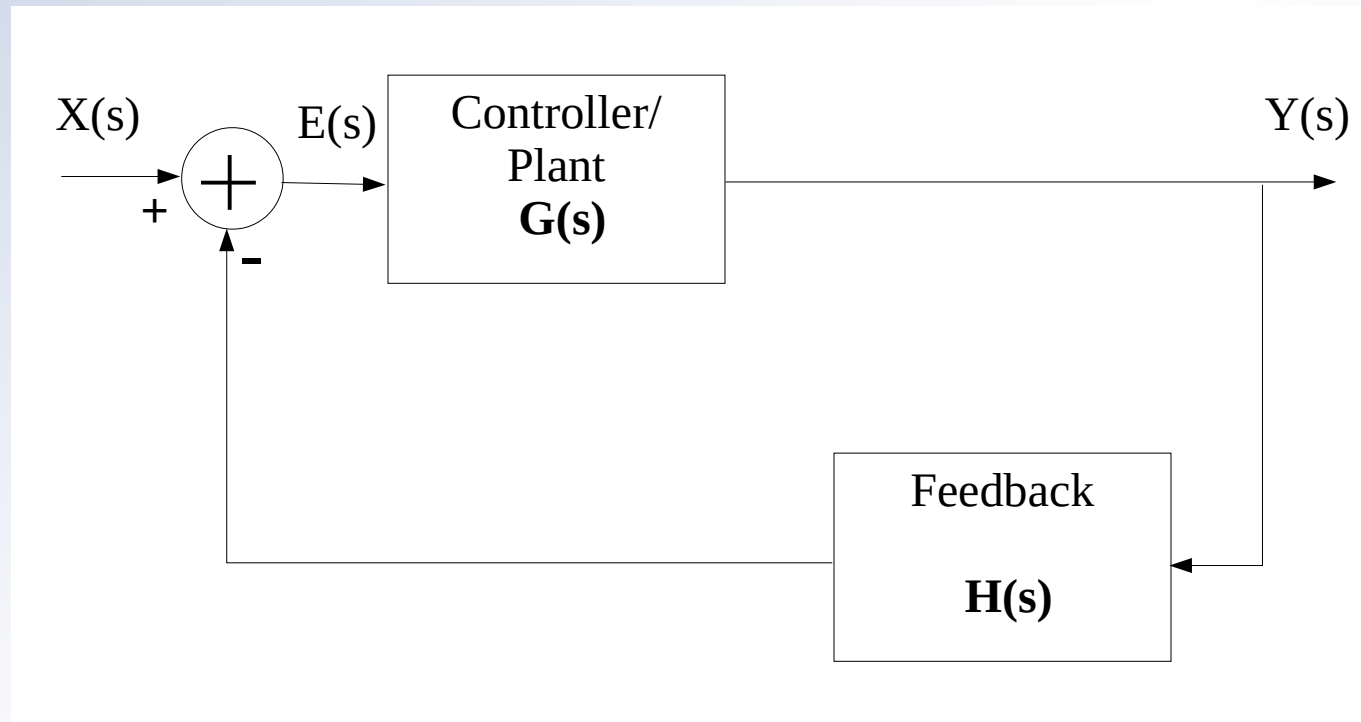

$$\frac{Y(s)}{X(s)} = \frac{G(s)}{1 + G(s)H(s)}$$

Basic Amplifier with Adjustable Gain

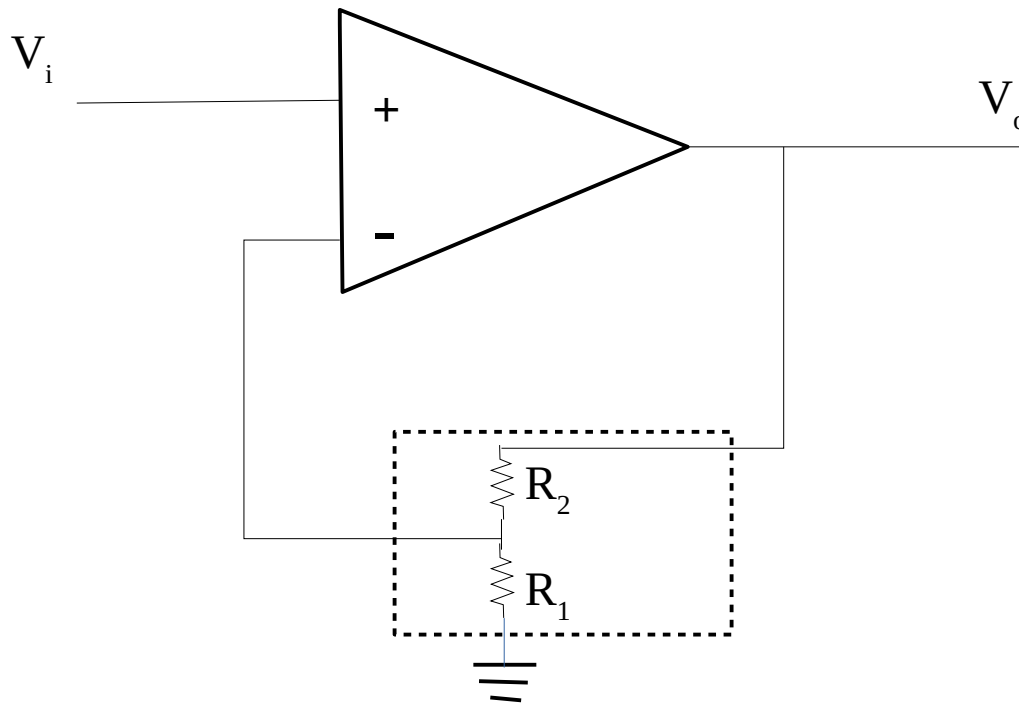


$$\begin{aligned}\frac{V_o}{V_i} &= \frac{A}{1 + A \cdot R_1 / (R_1 + R_2)} \\ &= \frac{1}{1/A + R_1 / (R_1 + R_2)} \\ &\approx 1 + \frac{R_2}{R_1} \quad \text{as } A \rightarrow \infty\end{aligned}$$

Simple Analysis of Op-Amp Circuits


- Due to high input impedance the current into amplifier at the two inputs is zero
- From the above point, the effective potential difference between the two inputs is zero (“virtually connected” or concept of “virtual ground”)
- The output is: $V_o = (V_a - V_b)G$, with $G \rightarrow$ very large

Inverting Amplifier

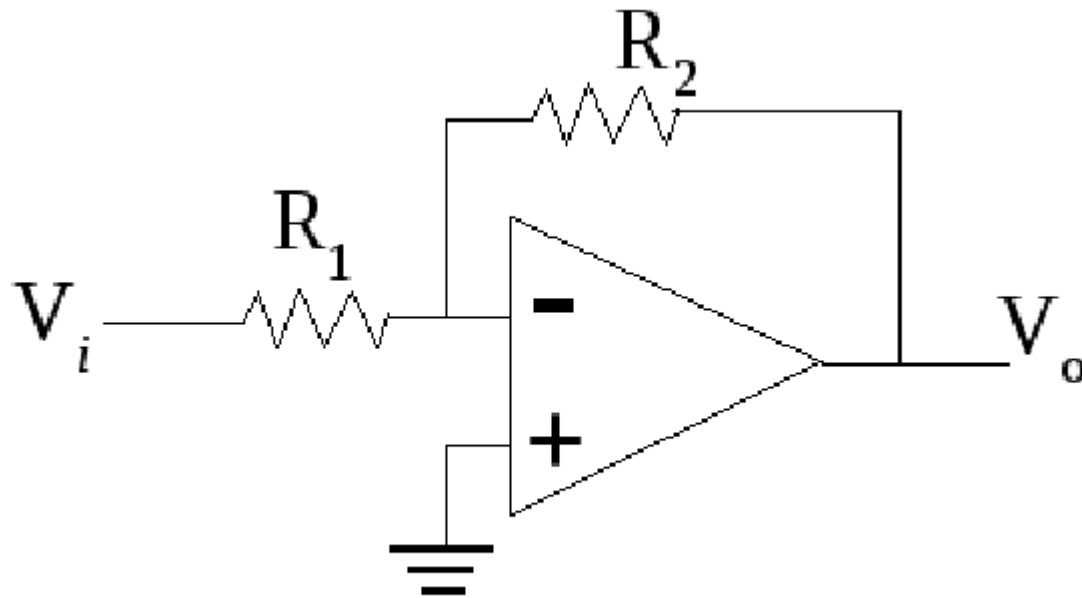


$$\frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

Differential Amplifier

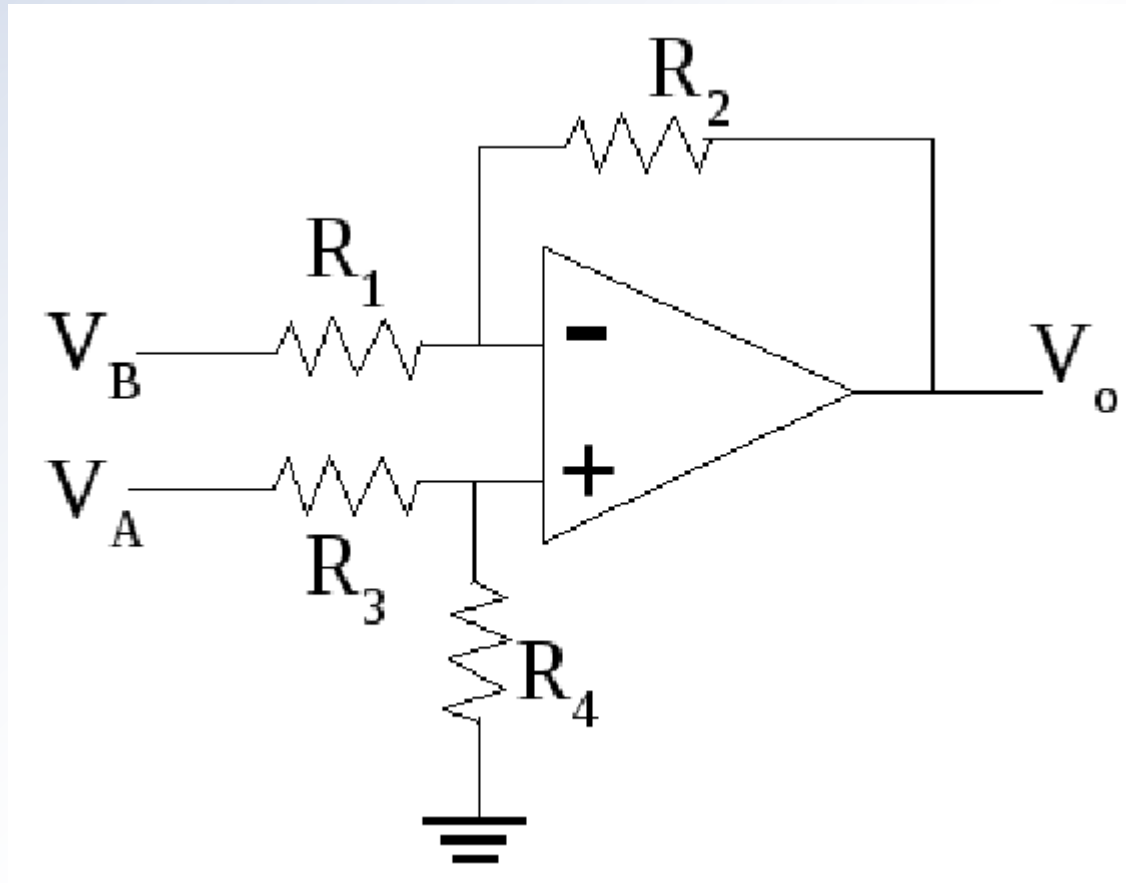


Low-Pass Filter

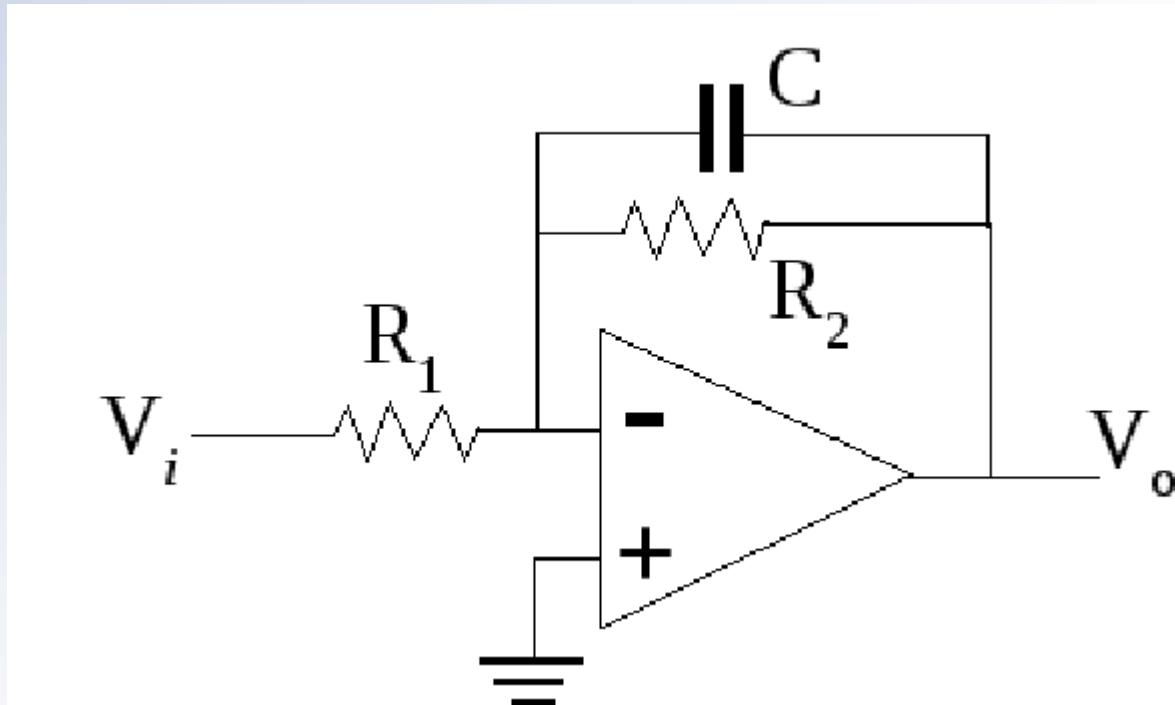


$$\frac{V_o(s)}{V_i(s)} = \frac{-R_2 \parallel C}{R_1} = \frac{-R_2/R_1}{1 + R_2Cs}$$

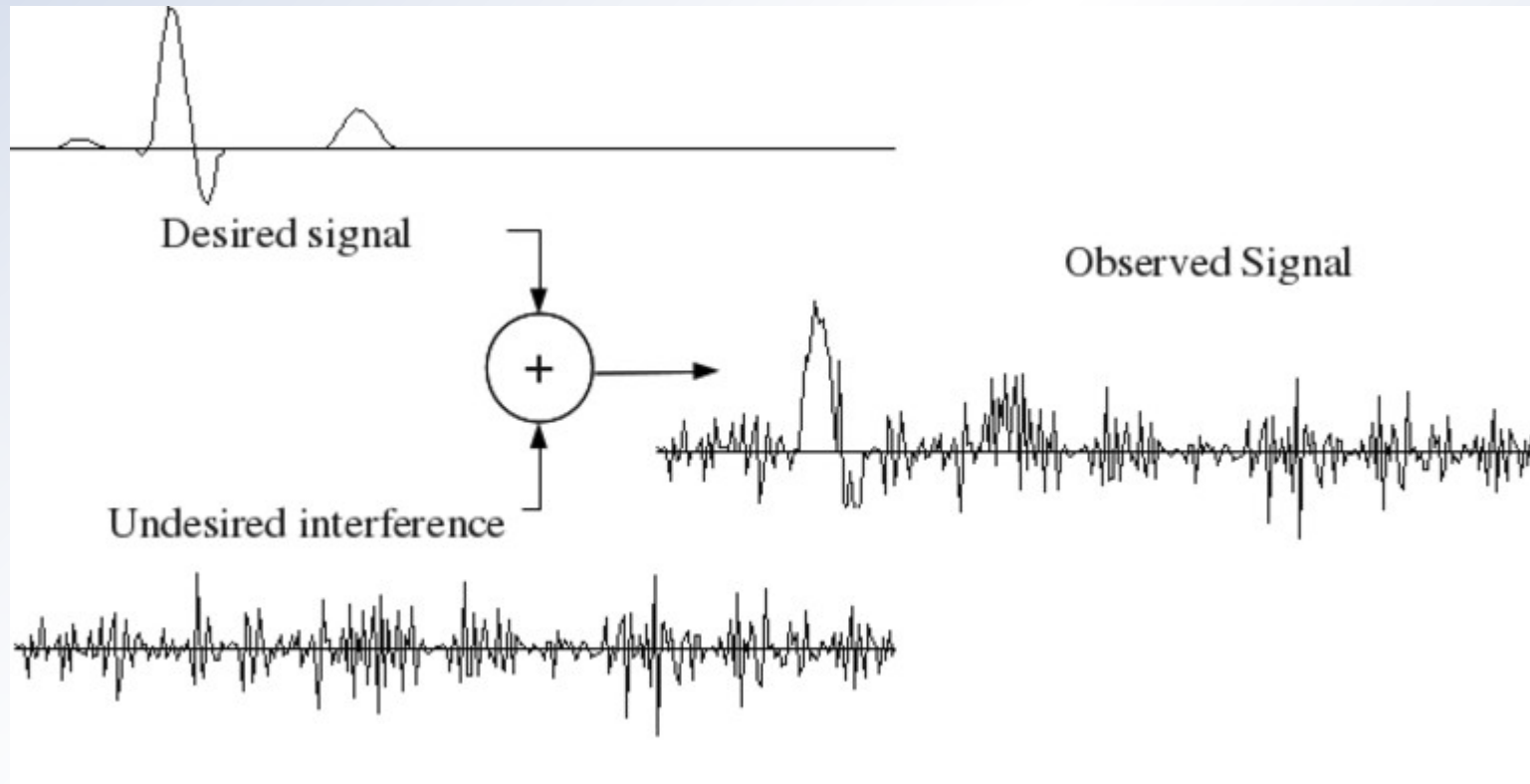
Signal contaminated by noise distinctly separated in frequency



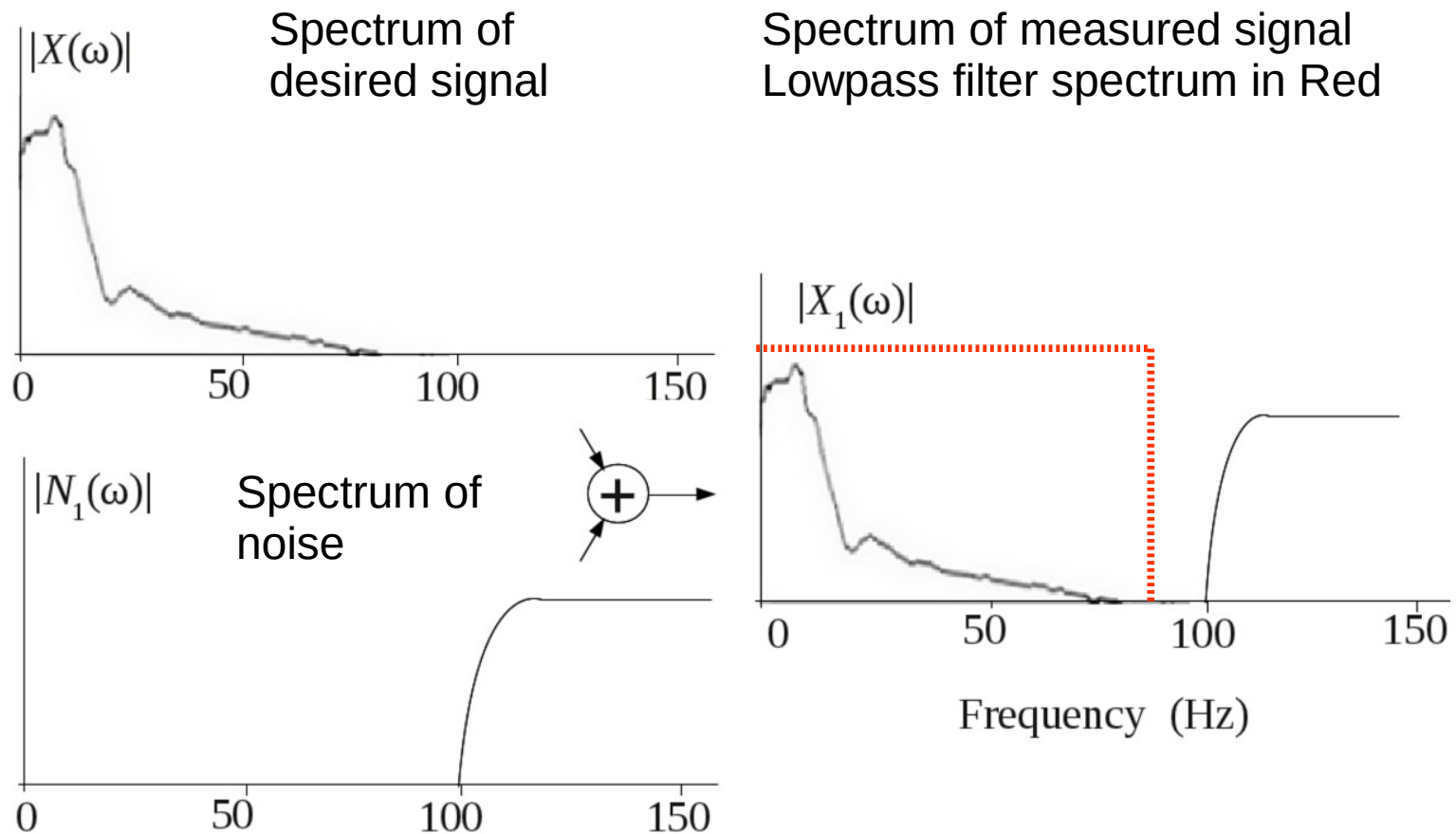
Lowpass filtering of distinct high frequency noise



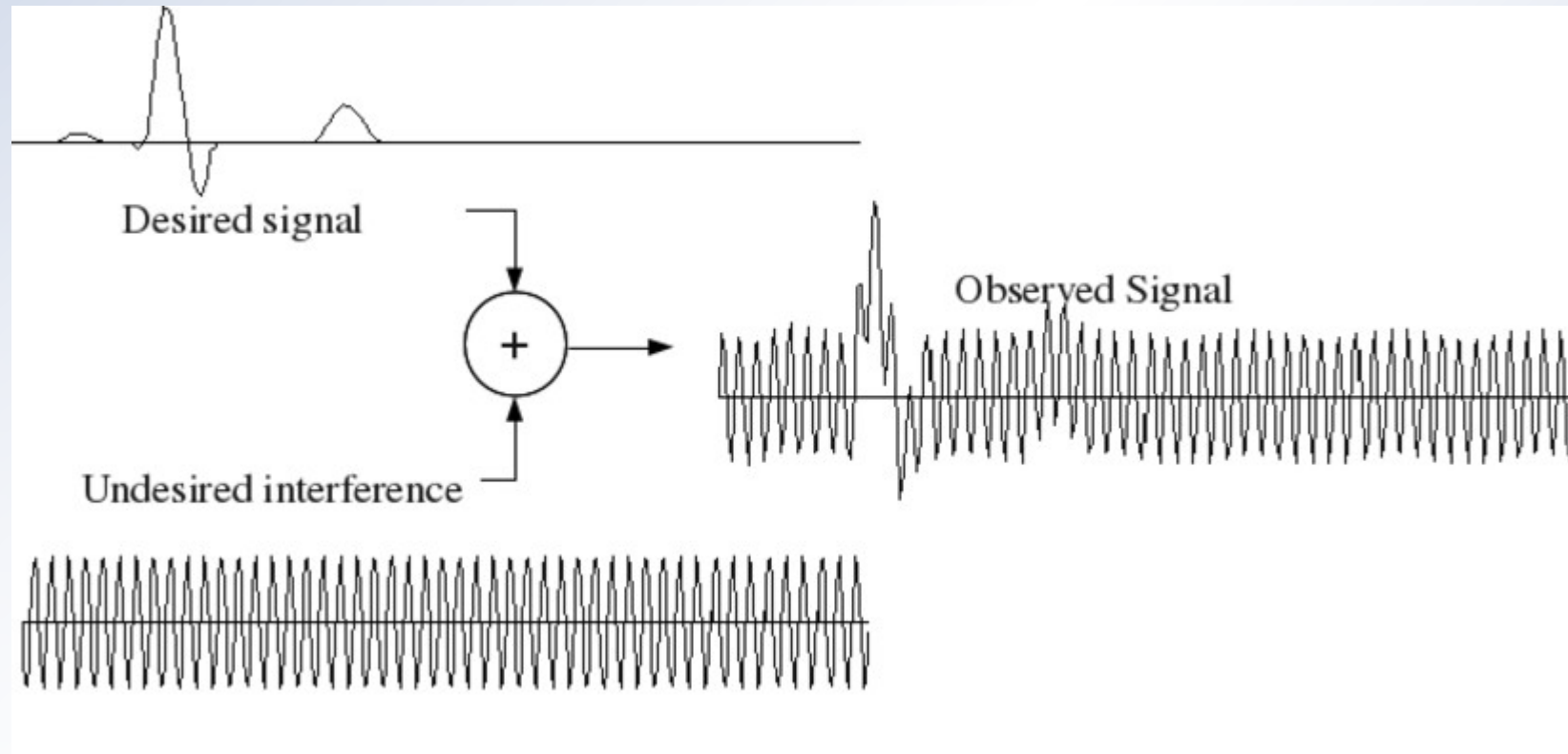
Signal contaminated by noise overlapping in frequency



Filtering Overlapping Noise

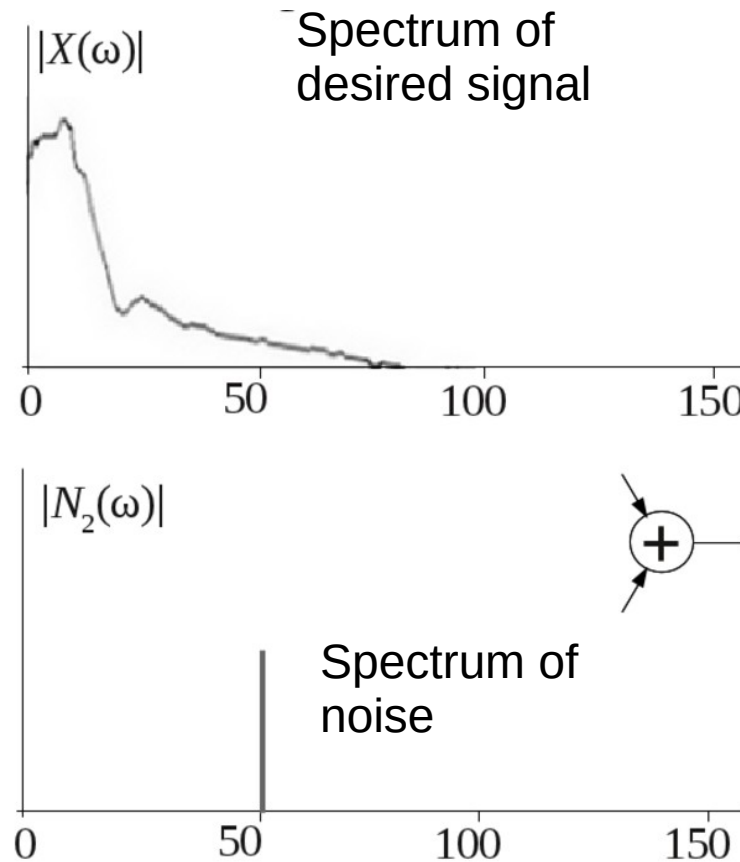

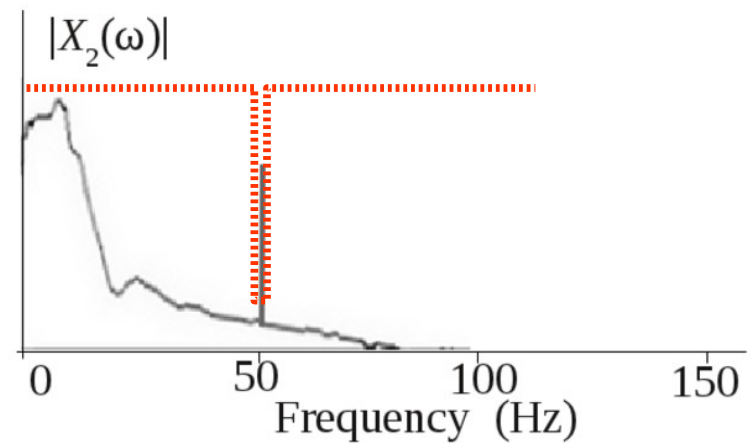Spectrum of measured signal
Optimal filter spectrum in Red




Optimal Filter - I

- Keep as much of the signal as possible
- Remove as much of the noise as possible
- This means:
 - In the frequencies where the signal and noise overlap, the filter attenuation is proportional to the ratio of signal to noise
 - In the frequencies where they don't overlap, keep all the signal and remove all the noise

Optimal Filter - II

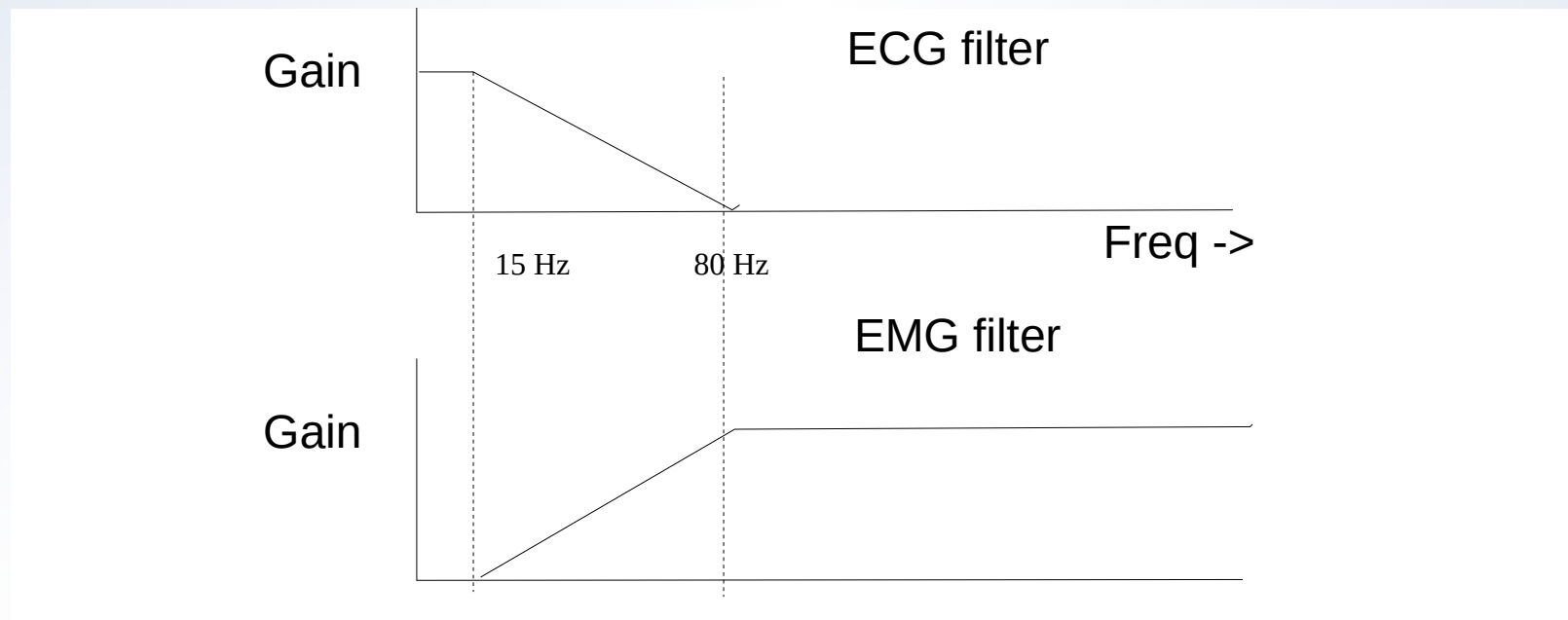- Consider the EMG and ECG both of which can be picked up simultaneously by electrodes on the chest
 - ECG spectrum: 0.05Hz-80Hz
 - EMG spectrum: 15Hz-300Hz



Cascading Filters

- The Laplace Transform converts the input-output relation in simple algebraic terms – i.e., only multiplications and divisions
- Multiple filters can be cascaded, and the cumulative effect is a multiplication of the individual input-output relations

Real Filters

- Real-time and offline filtering
- Implementation
 - Physical filters/Electrical – online/realtime
- Physical filters and online filters
 - Causal , cannot use future data
 - Have finite phase shift or time lag
- Offline filters (Digital Filters)
 - Can use “virtual future” data that has been stored

Phase shift in filters

- Phase shift can disrupt time relations in waveforms
- Phase shift can introduce lag between synchronous signals
- Linear phase filters introduce constant time lag to all frequencies
- Time lag: $\tau = \frac{\phi}{\omega}$ where ϕ is the phase shift and ω is the frequency

Characterizing Filters

- Frequency response
- Step response