




Sample Problems

Suresh Devasahayam
Department of Bioengineering
Christian Medical College, Vellore

Lecture - Outline

- Operational Amplifier Circuits
 - Sum and difference amplifier
 - Low-pass and high-pass filters
- Sensors with feedback compensation
 - Force sensor dynamic characteristics
 - Feedback compensation

Problem 1: Sum and Difference Amplifier

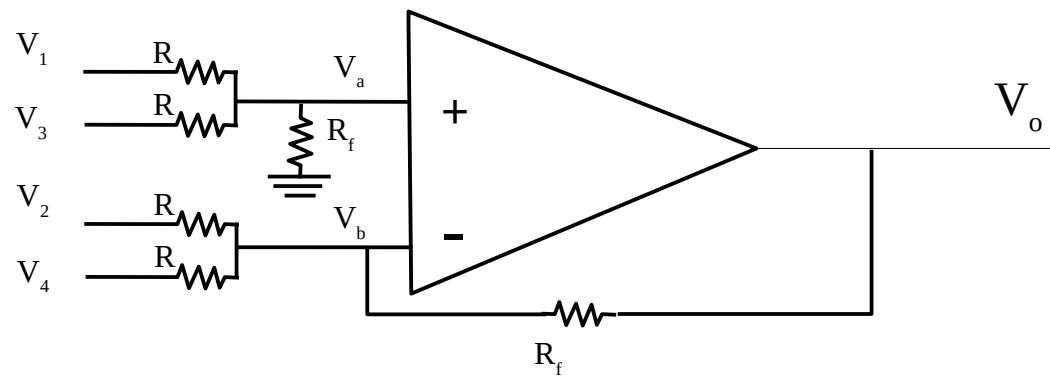

P1: Output of the sum-and-difference amplifier


$$V_a = \left(\frac{V_1 + V_3}{R} \right) \left(\frac{R R_f}{2R + R_f} \right)$$

$$V_b = \left(\frac{V_2 + V_4}{R} + \frac{V_o}{R_f} \right) \left(\frac{R R_f}{2R + R_f} \right)$$

$$V_a = V_b$$

$$V_o = (V_1 + V_3 - V_2 - V_4) \left(\frac{R_f}{R} \right)$$

Problem 2: Low-pass filter

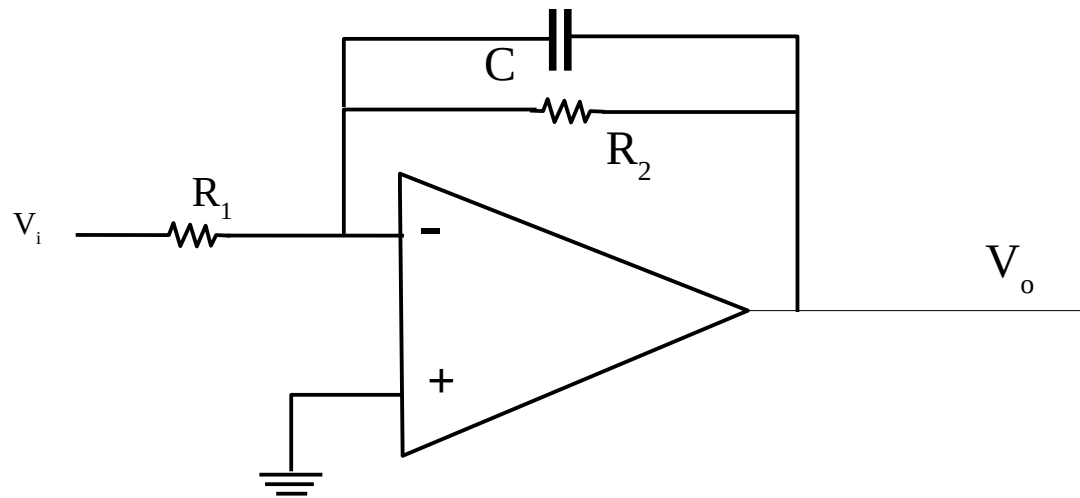

P2: Design the filter for a cutoff of 20Hz

$$\frac{V_o(s)}{V_i(s)} = \frac{-(R_2/R_1)}{1+R_2Cs}$$


$$R_1=R_2=10\text{ k}\Omega, \quad C=0.8\mu\text{F}, \quad f_c=20\text{ Hz}, \quad \omega_c=125\text{ rad/s}$$

$$\left| \frac{V_o(j\omega)}{V_i(j\omega)} \right| = \frac{1}{\sqrt{1+(RC\omega)^2}} = \frac{1}{\sqrt{1+(\omega/125)^2}}$$

P2:

f	ω	Magnitude	Magnitude (dB)	Phase
0.2	1.25	1	0	0
2.0	12.5	1	0	
20	125	0.707	-3	45
200	1250	0.1	-20	
2000	12500	0.01	-40	90

Problem 3: High-pass filter

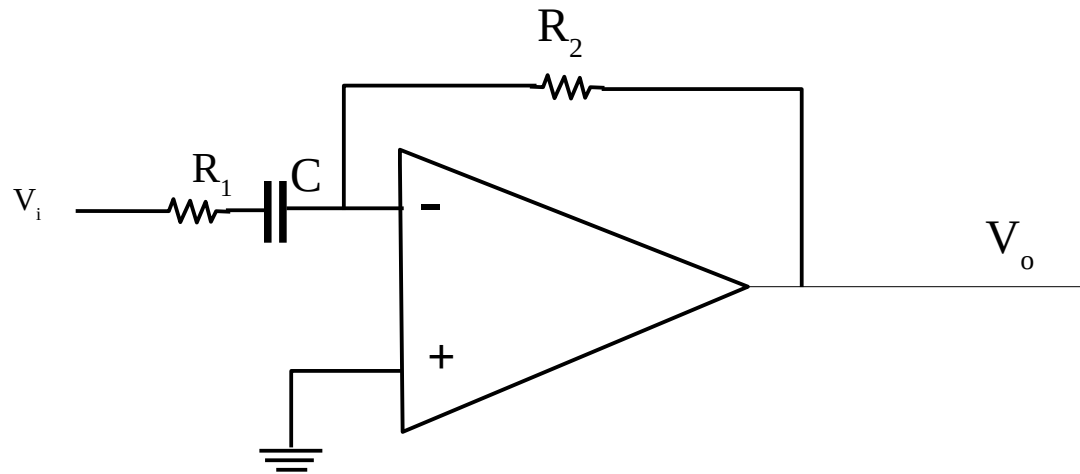

P3: Design the HPF with cutoff freq of 20Hz

$$\frac{V_o(s)}{V_i(s)} = \frac{-R_2Cs}{1+R_1Cs}$$


$$R_1=R_2=10k\Omega, \quad C=0.8\mu F, \quad f_c=20\text{ Hz}, \quad \omega_c=125\text{ rad/s}$$

$$\left| \frac{V_o(j\omega)}{V_i(j\omega)} \right| = \frac{RC\omega}{\sqrt{1+(RC\omega)^2}} = \frac{\omega/125}{\sqrt{1+(\omega/125)^2}}$$

P3:

f	ω	Magnitude	Magnitude (dB)	Phase
0.2	1.25	0.01	-40	
2.0	12.5	0.1	-20	
20	125	0.707	-3	
200	1250	1	0	
2000	12500	1	0	

P4: Force sensor

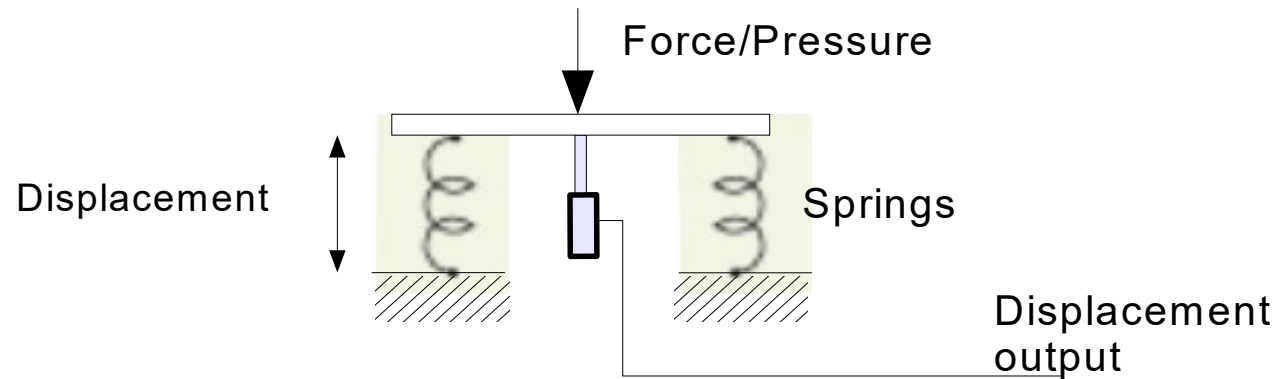

Mass: $m=100\text{g}$,
spring constant: $K=25.6\text{ N/m}$
viscous damping $B=0.8\text{ N.s/m}$

P4:


$$F(t) = m \frac{d^2 x(t)}{dt^2} + B \frac{dx}{dt} + Kx$$

$$V_o(t) = g_a x(t)$$


$$\frac{V_o(s)}{F_1(s)} = \frac{g_a}{ms^2 + Bs + K} = \frac{g_a/K}{(m/K)s^2 + (B/K)s + 1}$$

$$\frac{V_o(s)}{F_1(s)} = \frac{A}{\frac{s^2}{\omega_n^2} + 2\frac{\zeta}{\omega_n}s + 1}, \quad \omega_n = 16 \text{ r/s}, \quad \zeta = 0.25$$


P4: Sensor Frequency response

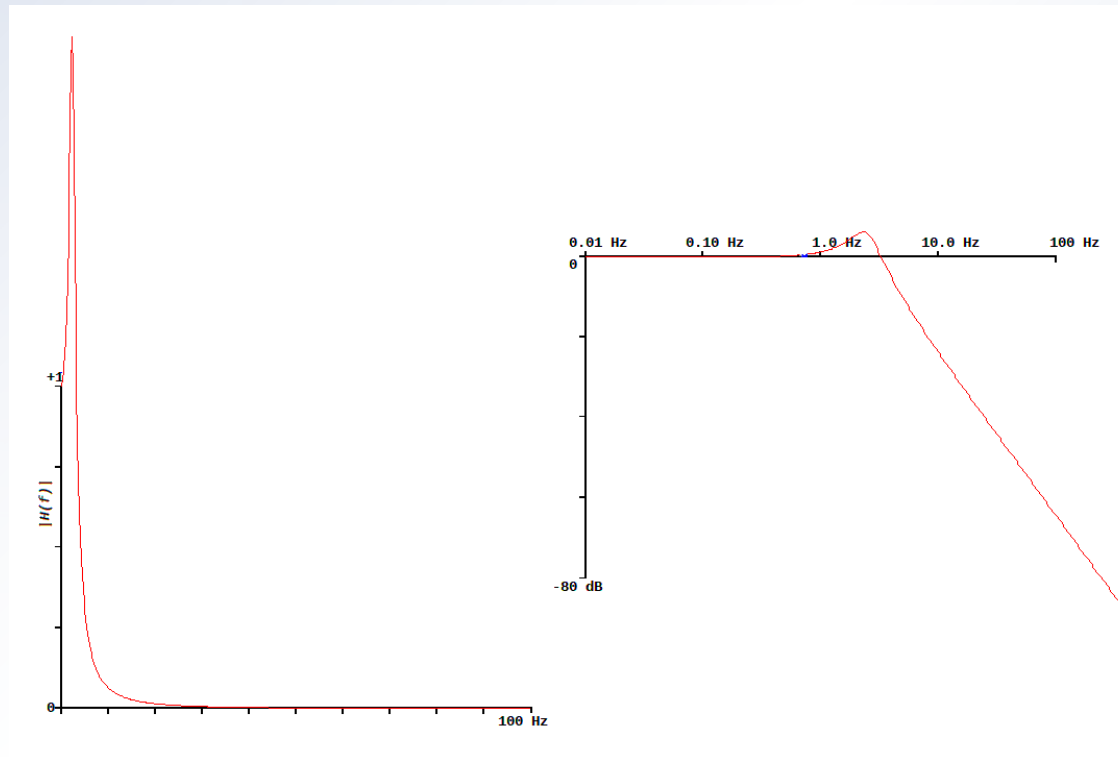


P4: Sensor Step response

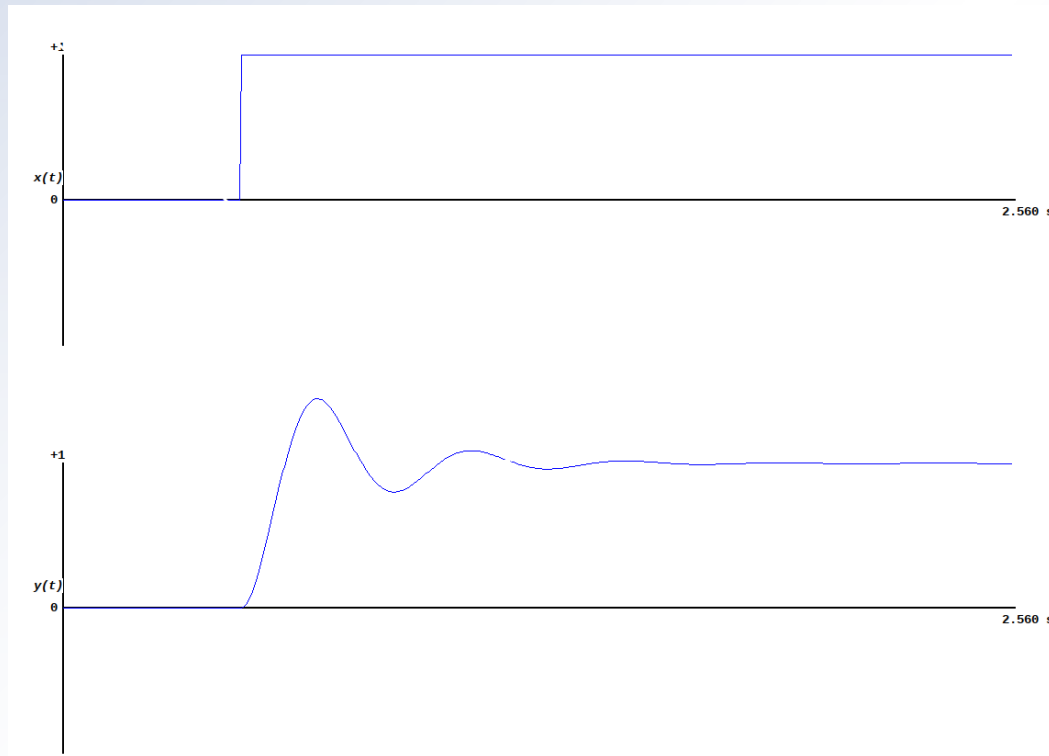

P4: Sensor with feedback compensation

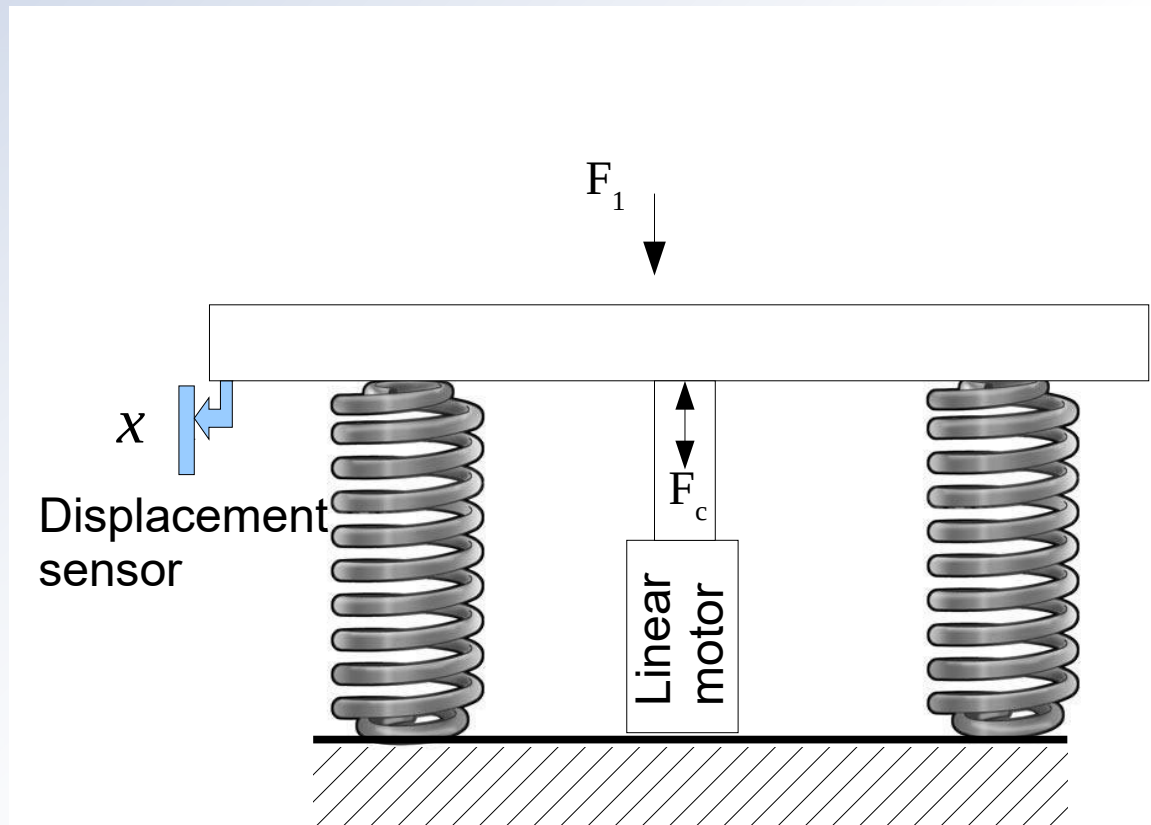

P4: Feedback compensation

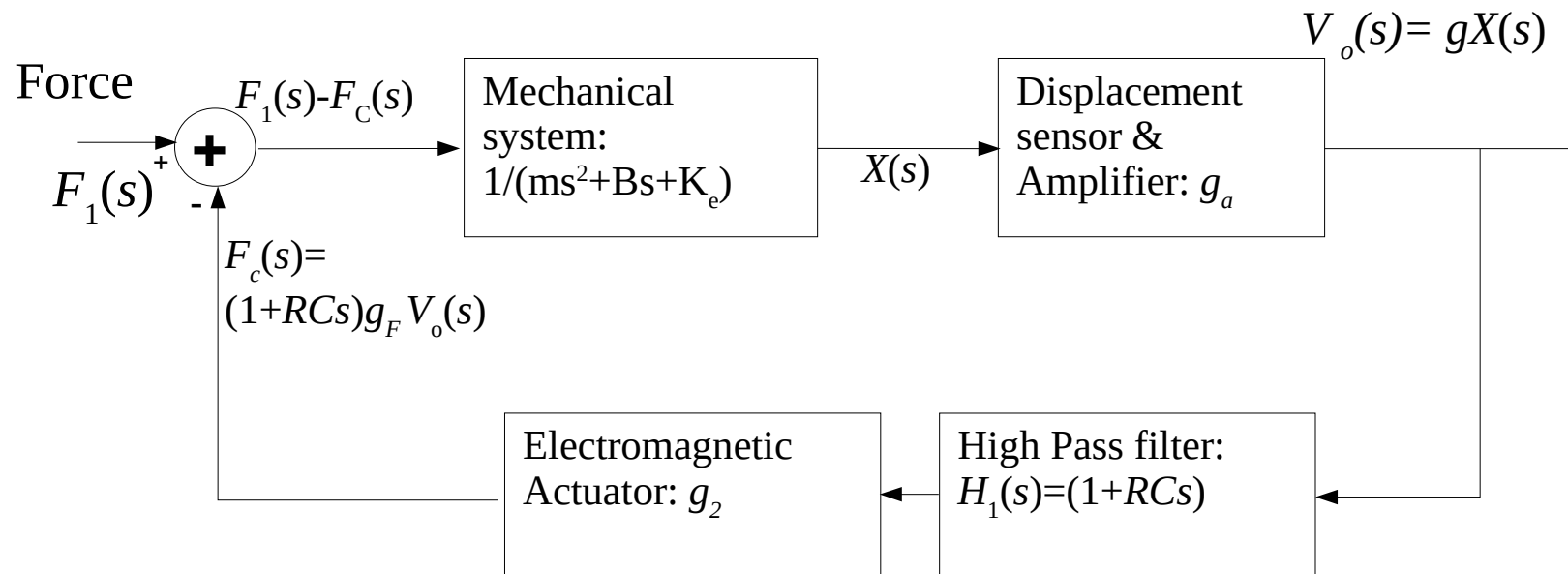

P4: Transfer function of sensor with feedback compensation


$$\frac{V_o(s)}{F_1(s)} = \frac{g_a}{ms^2 + (B + g_a g_2 RC)s + (K + g_a g_2)}$$

$$\frac{V_o(s)}{F_1(s)} = \frac{A}{\frac{s^2}{\omega_c^2} + 2\frac{\zeta}{\omega_c}s + 1}$$


$$A = \frac{g_a}{K + g_a g_2} \quad \omega_c = \sqrt{\frac{K + g_a g_2}{m}} \quad \zeta = \frac{B + g_a g_2 RC}{\sqrt{4m(K + g_a g_2)}}$$

$$g_a g_2 = 76.8, \quad RC = 0.073, \quad \omega_n = 32 \text{ r/s} = 5.08 \text{ Hz}, \quad \zeta = 1.0$$

P4: Compensated Sensor Freq Response

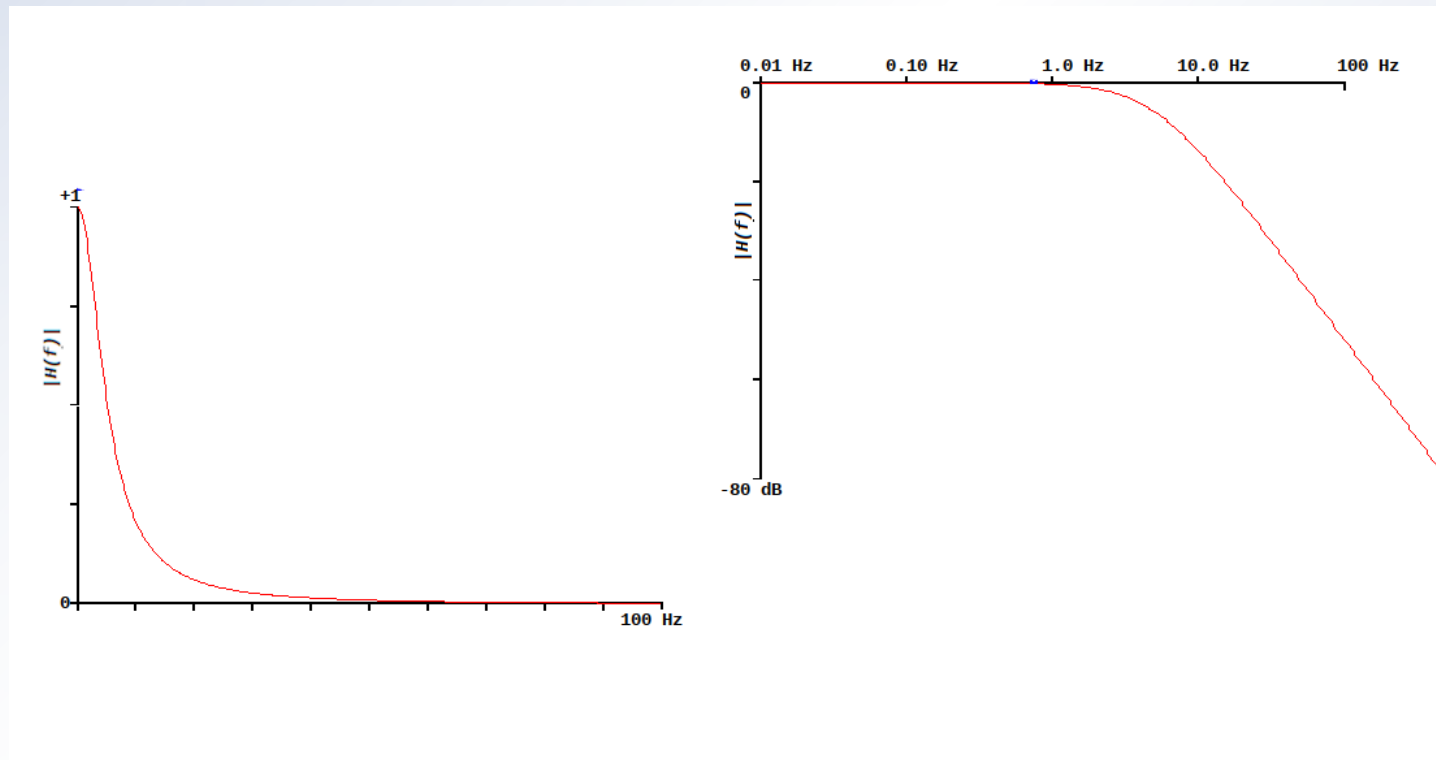

P4: Compensated Sensor Step Response

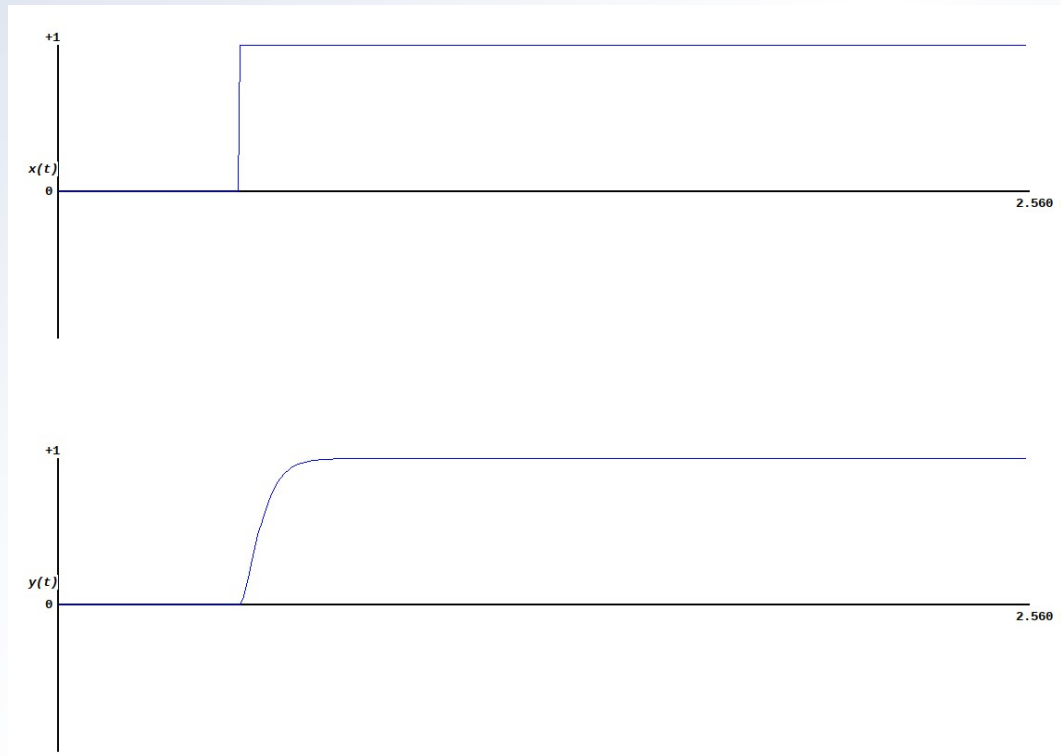

End of Lecture