




Resistive Transduction

Suresh Devasahayam
Department of Bioengineering
Christian Medical College, Vellore

Lecture - Outline

- Variable Resistance Potentiometer as Transducer
- Power and Error in Potentiometer measurement
- Measuring Small Resistance Changes
 - Bridge Measurement
 - Single Active Arm Bridge
- Temperature compensation
 - Two and Four Active Arm bridge

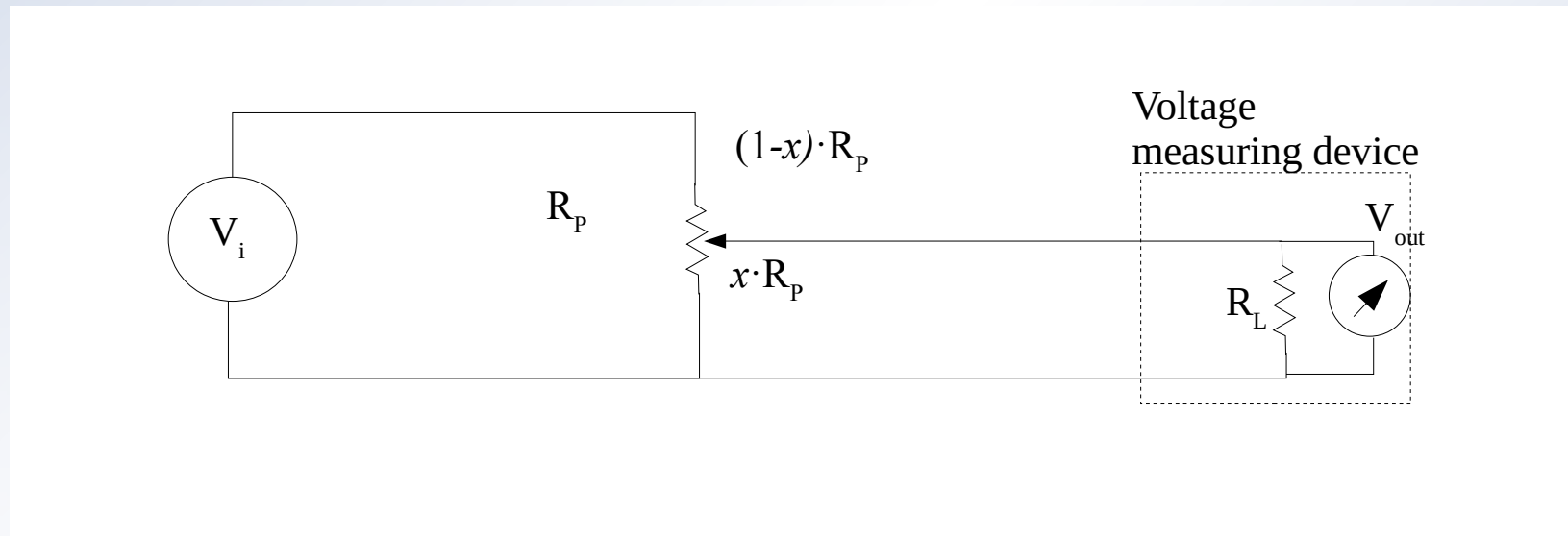Displacement measurement with a potentiometer



Simple case

$$V_{out} = \frac{V_i}{R_P} \cdot x R_P$$

$$\frac{V_{out}}{V_i} = x$$

Simple case:

- If $R_L \gg R_p$:

$$V_{out} = \frac{V_i}{R_p} \cdot x R_p \quad \frac{V_{out}}{V_i} = x$$

- Current drawn by R_p :

$$I_p = \frac{V_i}{R_p}$$

- Power dissipated:

$$Power_p = \frac{V_i^2}{R_p}$$

- To minimize power dissipated in the potentiometer, the value of R_p **should be large.**

Considering the value of the measuring instrument

- R_p is large :

$$V_{out} = I_{R_L} \cdot R_L = \frac{V_i}{\left((1-x)R_p + \frac{xR_p R_L}{xR_p + R_L} \right)} \cdot \left(\frac{xR_p}{xR_p + R_L} \right) R_L$$

$$\frac{V_{out}}{V_i} = \frac{xR_L}{xR_p(1-x) + R_L}$$

- R_L and R_p are large:

$$\alpha = \frac{R_L}{R_p}$$


$$\frac{V_{out}}{V_{\%in}} = \frac{x\alpha}{x(1-x) + \alpha}$$

- Measurement error:

$$Error = \frac{Actual\ value - Desired\ value}{Desired\ value} = \frac{\left(\frac{x\alpha}{x(1-x) + \alpha} \right) - x}{x} = \frac{-x(1-x)}{\alpha + x(1-x)}$$

Bridge Measurement


Measuring small resistance change

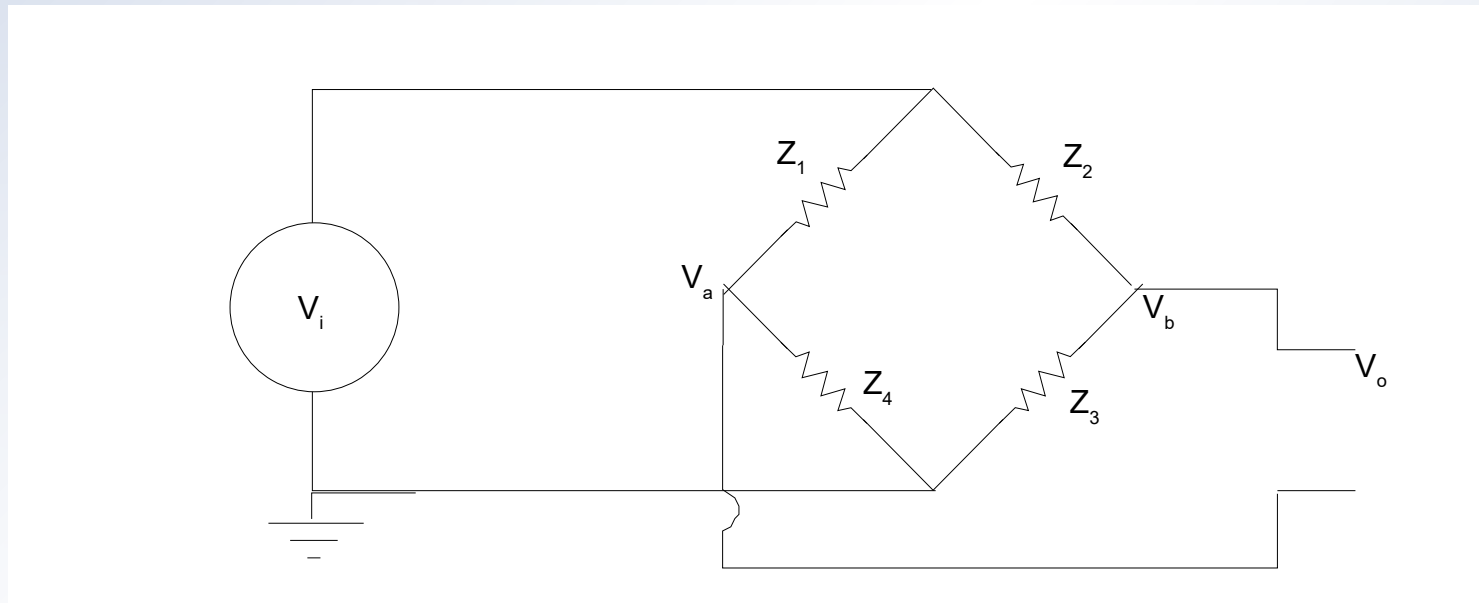

$$V_o = V_a - V_b = V_i \left(\frac{Z_4}{Z_1 + Z_4} - \frac{Z_3}{Z_2 + Z_3} \right)$$

Measuring the bridge output

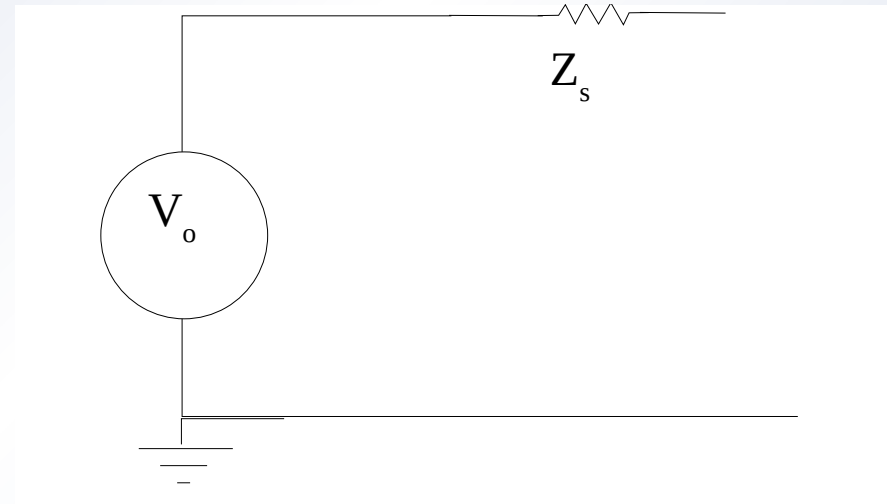- Thevenin equivalent of the bridge
- Output impedance or source impedance = OC voltage/SC current



$$Z_s = \frac{Z_1 Z_2}{Z_1 + Z_2} + \frac{Z_3 Z_4}{Z_3 + Z_4}$$

One Active Arm Bridge

- A resistive transducer's resistance varies around a “no signal” value of “R”

$$Z_4 = R \pm \Delta R = R(1 \pm \Delta), \quad Z_1 = Z_2 = Z_3 = R$$

$$V_o = V_i \frac{\Delta}{4 + 2\Delta} \approx V_i \frac{\Delta}{4}, \quad Z_s = R \frac{(4 + 3\Delta)}{(4 + 2\Delta)} \approx R$$

Two active arm bridge

- Resistance also has a temperature dependence
- If transduction can yield complementary resistance change, then we can use a two active arm bridge:

$$Z_4 = R(1 + \Delta_s + \Delta_T), \quad Z_3 = R(1 - \Delta_s + \Delta_T), \quad Z_1 = Z_2 = R$$

$$V_o = V_i \left\{ \frac{R(1 + \Delta)}{R(2 + \Delta)} - \frac{R(1 - \Delta)}{R(2 - \Delta)} \right\}$$

$$V_o = V_i \left\{ \frac{(1 + \Delta)(2 - \Delta) - (1 - \Delta)(2 + \Delta)}{(4 - \Delta^2)} \right\} =$$

$$V_o \approx V_i \frac{\Delta}{2}, \quad Z_s = R \left(1 - \frac{\Delta^2}{2} \right)$$