



Electrical Impedance

Suresh Devasahayam
Department of Bioengineering
Christian Medical College, Vellore

Lecture - Outline

- Resistive and Reactive Elements
- Laplace and Fourier Transforms
- Measuring Impedance
- Transfer Function
- Amplifiers
- Operational Amplifiers

Laplace Transform and Fourier Transform

$$L\{x(t)\} = \int x(t) e^{-st} dt = X(s)$$

$$F\{x(t)\} = \int x(t) e^{-j\omega t} dt = X(j\omega)$$

- Properties of the Laplace Transform:
- Differentiation in time domain \Rightarrow multiply by s (or $j\omega$) in Transform domain
- Integration in time domain \Rightarrow multiply by $1/s$ (or $1/j\omega$) in Transform domain

Resistive and Reactive Elements – Time and Laplace

Resistance

$$V = R \cdot I$$

Inductance

$$V(t) = L \frac{dI(t)}{dt}$$

Capacitance

$$V(t) = \frac{1}{C} \int I(t) dt$$

Resistance

$$V(s) = R \cdot I(s)$$

Inductance

$$V(s) = L s \cdot I(s)$$

Capacitance

$$V(s) = \frac{1}{C s} \cdot I(s)$$

Impedance

- Impedance is the ratio of voltage to current in the Laplace domain or Fourier domain

$$Z(s) = \frac{V(s)}{I(s)}$$

$$Z(j\omega) = \frac{V(j\omega)}{I(j\omega)}$$

Calculating Impedance

- Resistor and capacitor in series

$$Z(s) = R + \frac{1}{Cs}$$


- R and C in parallel

$$Z(s) = \frac{R}{1 + RCs}$$

Measuring Impedance

- Simple method is to Measure with sinusoidal V, I
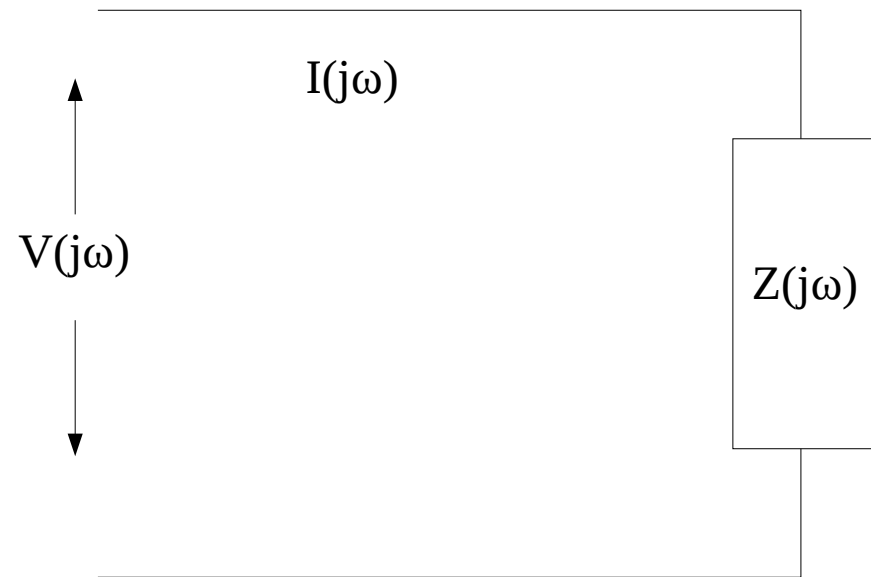
$$\frac{V(j\omega)}{I(j\omega)} = Z(j\omega)$$




Input-output Transfer ratio and Transfer function

- Input-Output relation
 - Purely real terms (e.g., resistance)
 - Includes Reactive terms
- Transfer function:
$$H(s) = \frac{\text{Output}}{\text{Input}}$$
- Measuring Transfer ratio

Input-output Transfer ratio

- Input-Output relation
 - Purely real terms (i.e., only resistance)
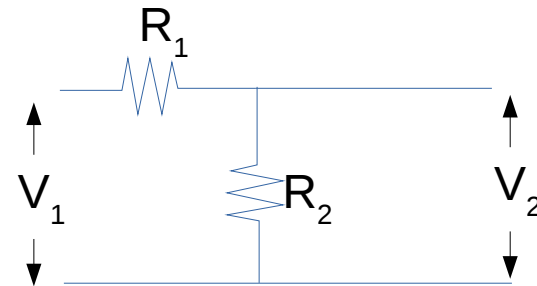
$$H = \frac{\text{Output}}{\text{Input}}$$



- Measuring Transfer ratio:

$$\frac{V_2}{V_1} = \frac{R_2}{R_1 + R_2}$$


Input-output Transfer Function

- Input-Output relation
 - Complex terms
(i.e., R, L, C)

$$H(s) = \frac{\text{Output}}{\text{Input}}$$

- Measuring Transfer ratio:
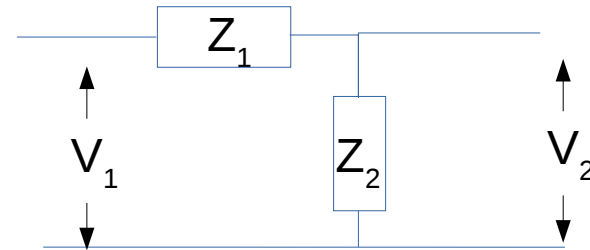
$$\frac{V_2(s)}{V_1(s)} = \frac{Z_2(s)}{Z_1(s) + Z_2(s)}$$




Input-output Transfer Function – High Pass Filter

- Transfer function of an RC filter – High Pass

$$\frac{V_2(s)}{V_1(s)} = \frac{R_2}{1/(C_1 s) + R_2} = \frac{R_2 C_1 s}{1 + R_2 C_1 s}$$

$$H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = \frac{R_2}{1/(C_1 j\omega) + R_2} = \frac{R_2 C_1 j\omega}{1 + R_2 C_1 j\omega}$$

$$|H(j\omega)| = \frac{R_2 C_1 \omega}{\sqrt{1 + (R_2 C_1 \omega)^2}}$$

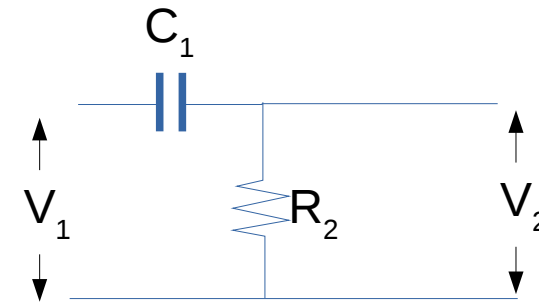


Input-output Transfer Function

- Transfer function of RC filter
 - Low Pass:

$$\frac{V_2(s)}{V_1(s)} = \frac{1/(C_2 s)}{R_1 + 1/(C_2 s)} = \frac{1}{1 + R_1 C_2 s}$$

$$H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = \frac{1/(C_2 j\omega)}{R_1 + 1/(C_2 j\omega)} = \frac{1}{1 + R_1 C_2 j\omega}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (R_1 C_2 \omega)^2}}$$

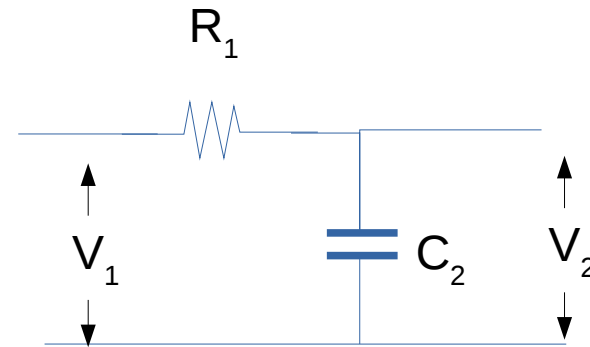

Attenuators and Amplifiers
