
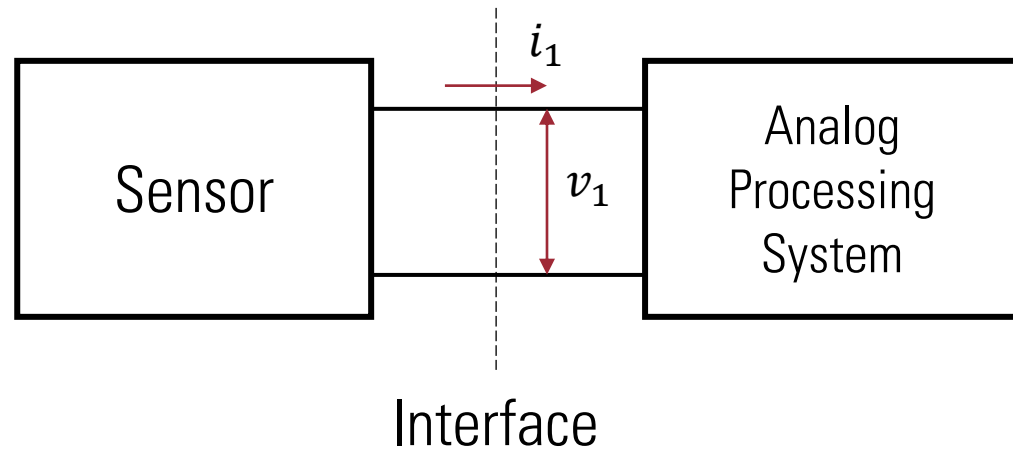


# Transducers & Instrumentation

Module 02


(Basic Instrumentation)

# A typical measurement system

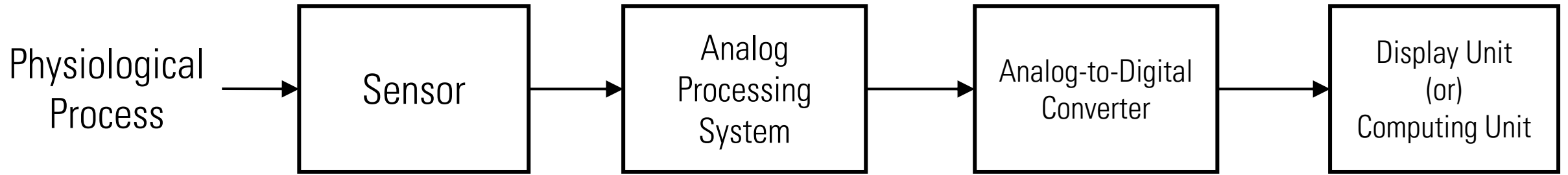

Amplification  
Attenuation  
Filtering  
Signal conversion  
.  
.  
.

# Basic (linear) Electrical Circuits

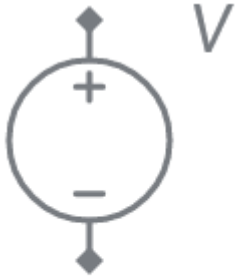

$$i(t) = \frac{v(t)}{R}$$



$$i(t) = C \frac{dv(t)}{dt}$$



$$i(t) = \frac{1}{L} \int_{-\infty}^t v(l) \cdot dl$$

# Linear Electrical Circuits – Frequency Domain Characteristics



$$i(t) = \frac{v(t)}{R}$$

$$I(\omega) = \frac{V(\omega)}{R}$$



$$i(t) = C \frac{dv(t)}{dt}$$




$$I(\omega) = j\omega C \cdot V(\omega)$$





$$i(t) = \frac{1}{L} \int_{-\infty}^t v(l) \cdot dl$$

$$I(\omega) = \frac{1}{j\omega L} V(\omega)$$

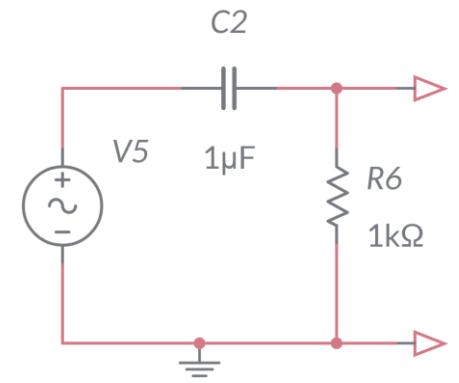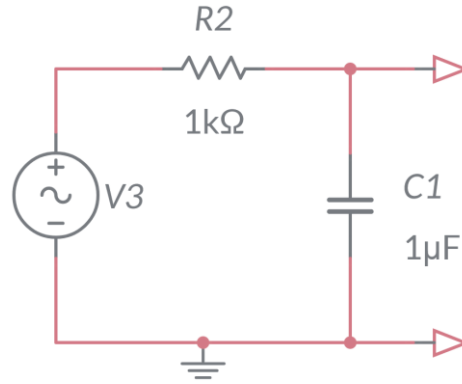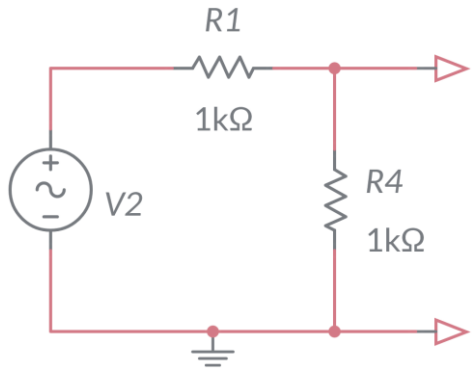
# Behaviour of some simple linear circuits




# Equivalent circuit

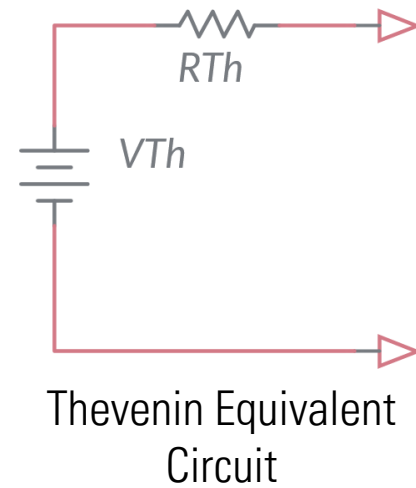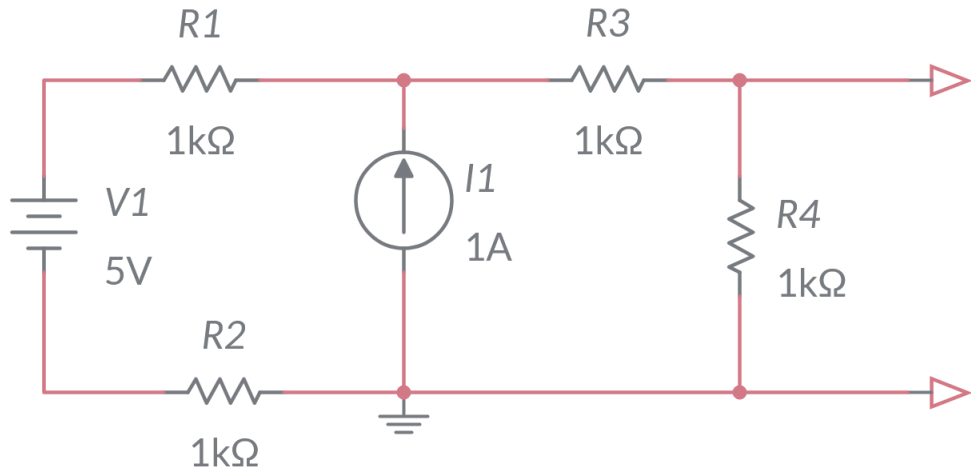

# Analog processing of sensor output

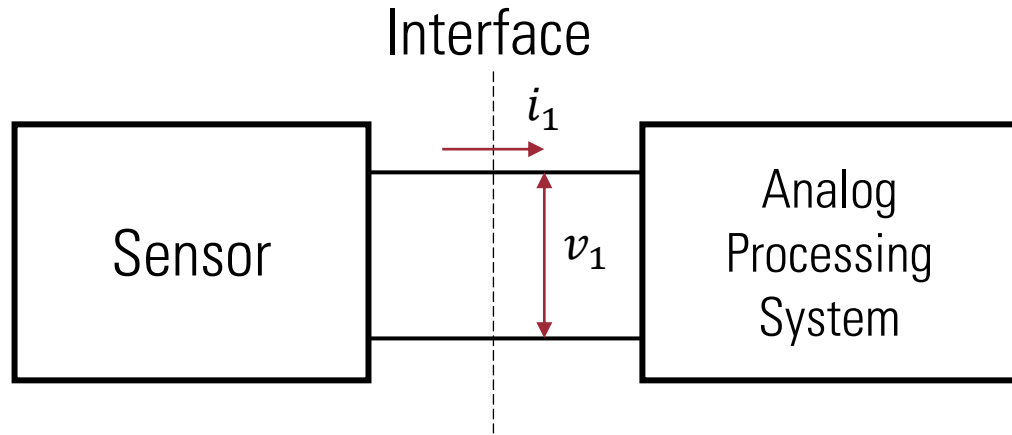


Sensor Equivalent Circuit

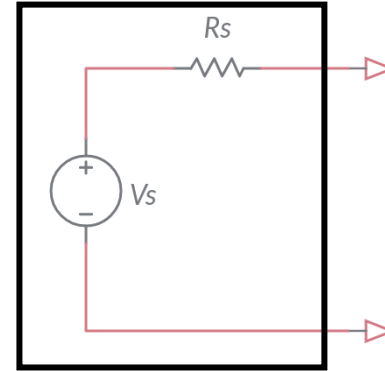

Sensor as seen by the analog processing system


Output Impedance

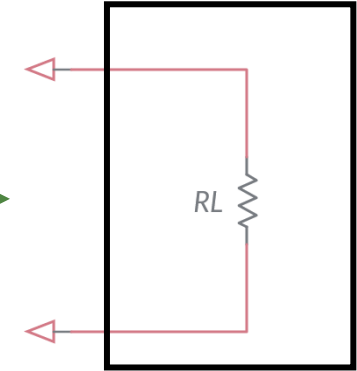

Analog processing circuit seen by the sensor


Input Impedance

# Analog processing of sensor output

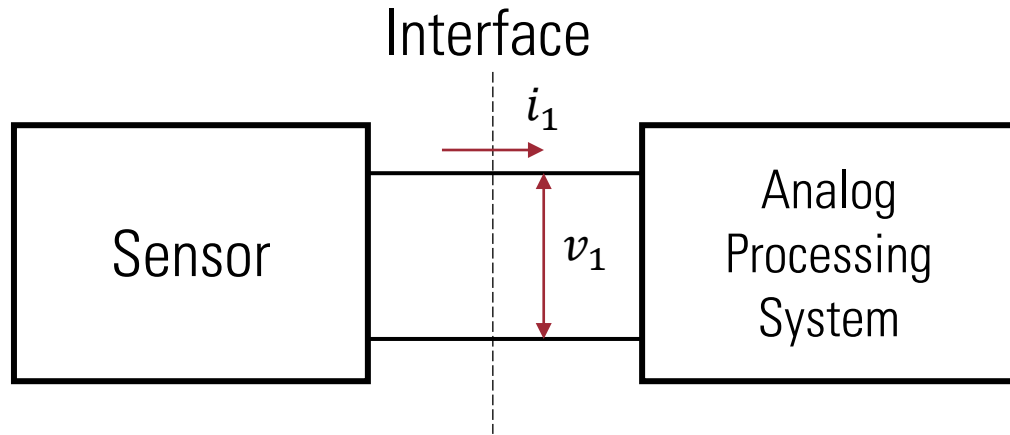

**Loading** occurs because of the finite input and non-zero output impedance

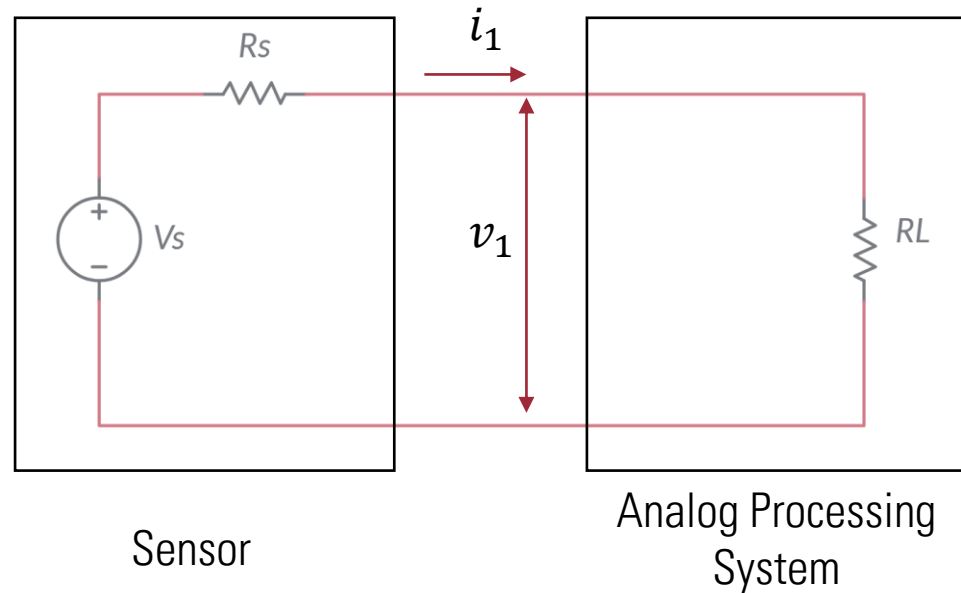
$$v_1 = \frac{R_L}{R_S + R_L} v_s \implies v_1 < v_s$$



How can we reduce loading?




# Analog processing: Amplifier

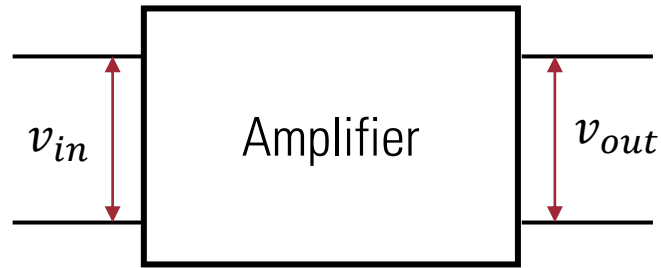


$$v_{out} = G \cdot v_{in}$$

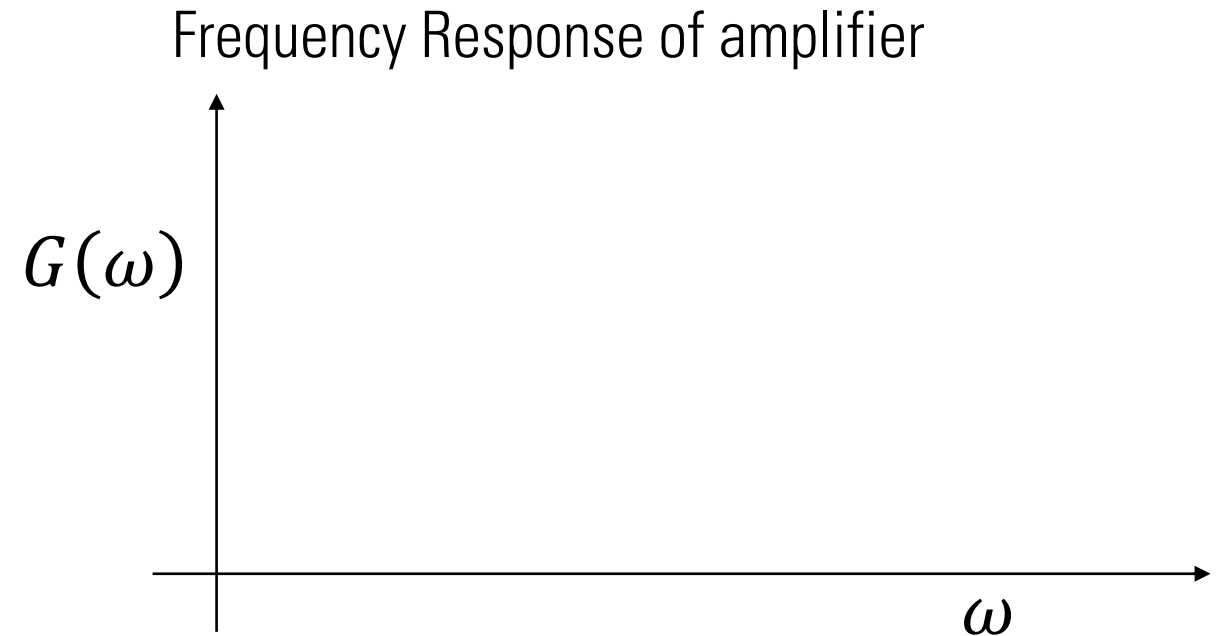
$$G_{dB} = 20 \cdot \log \left( \frac{v_{out}}{v_{in}} \right)$$



# Analog processing: Amplifier

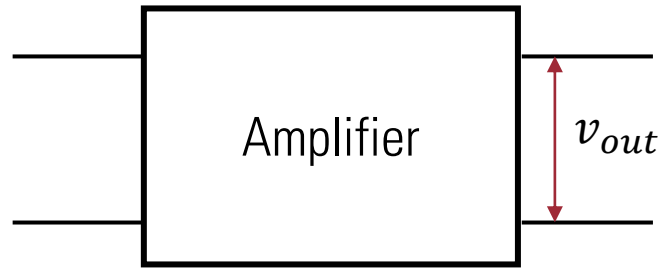


Loading in real amplifiers

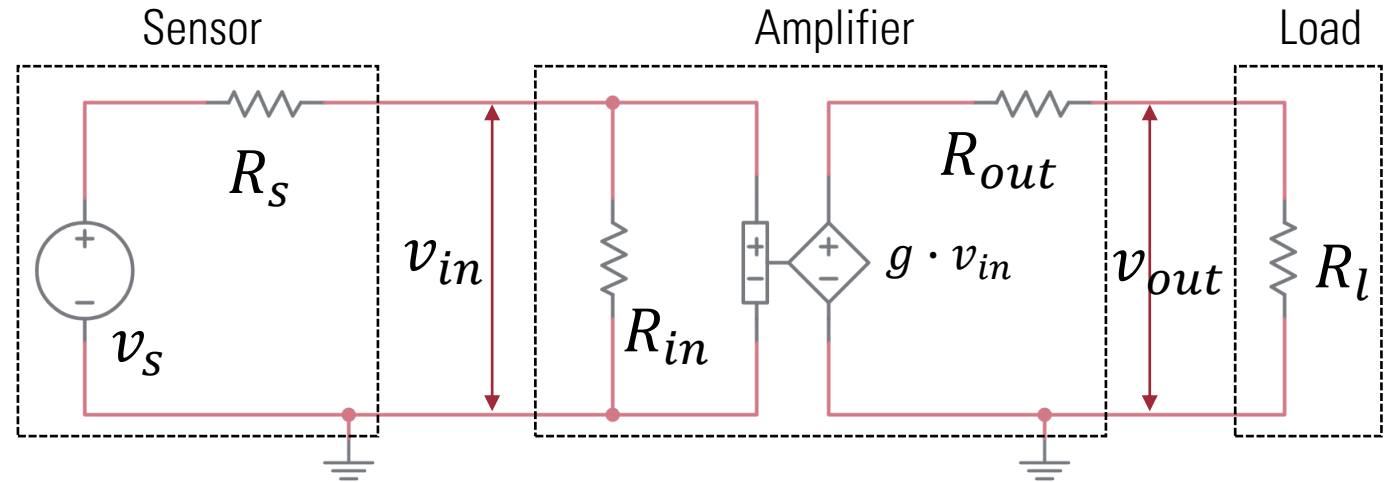
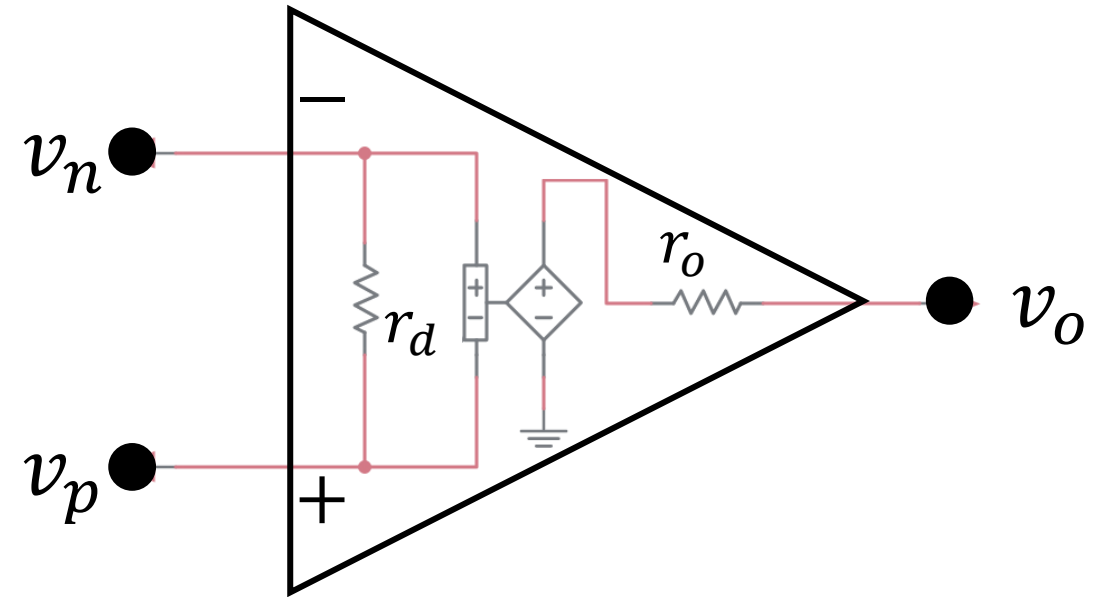
# Operational Amplifier

- Practical, low-cost, commonly available integrated circuit – Operational Amplifier (op-amp).
- An voltage amplifier with extremely high gain  $g$ .
- Has very high input impedance  $r_d$  and low output impedance  $r_o$ .

$$v_o = g \cdot v_d = g \cdot (v_p - v_n)$$




Ideal Op-amp

$$r_d = \infty$$


$$r_o = 0$$

$$g = \infty$$


# Operational Amplifier

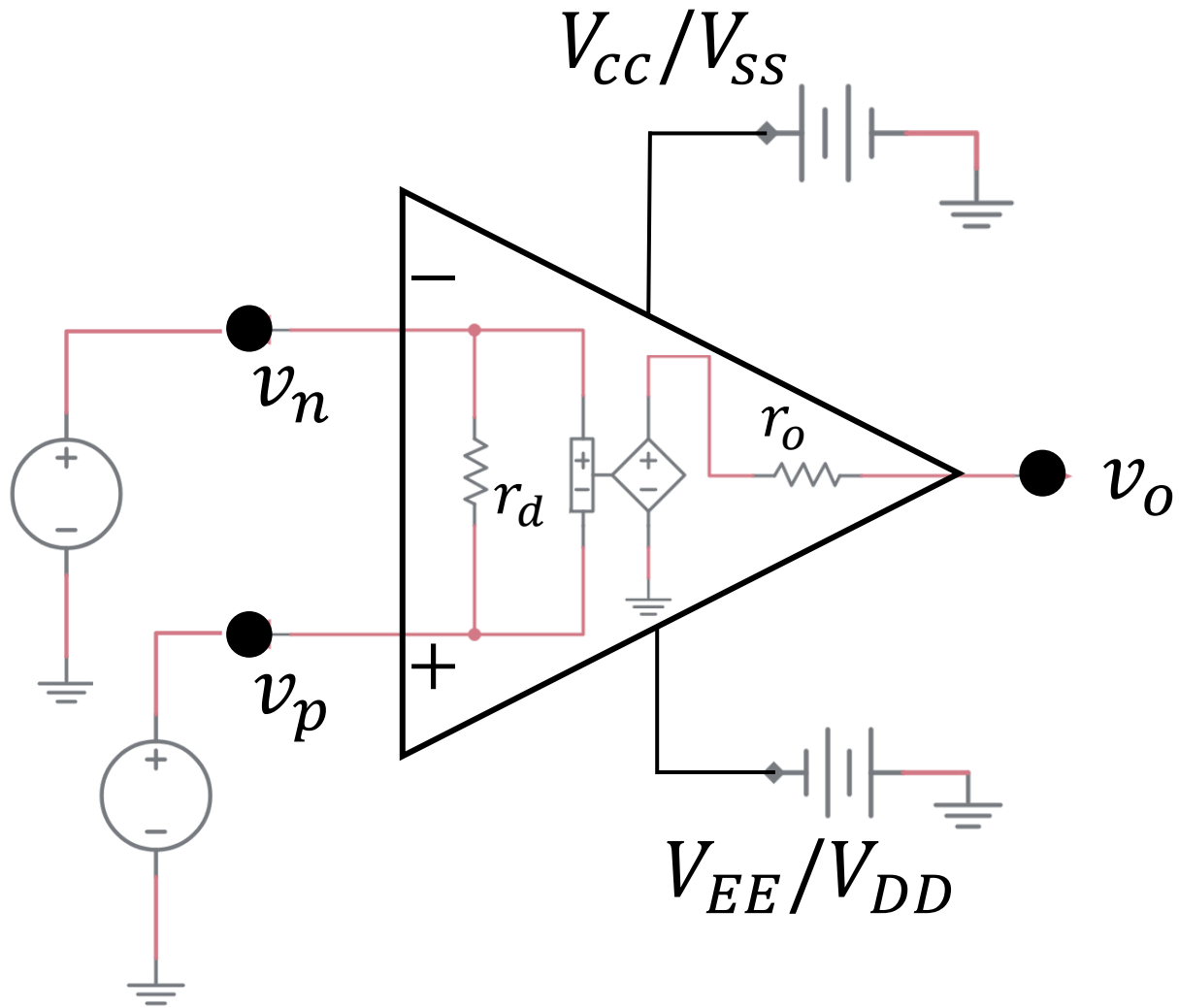


# Non-Inverting Amplifier

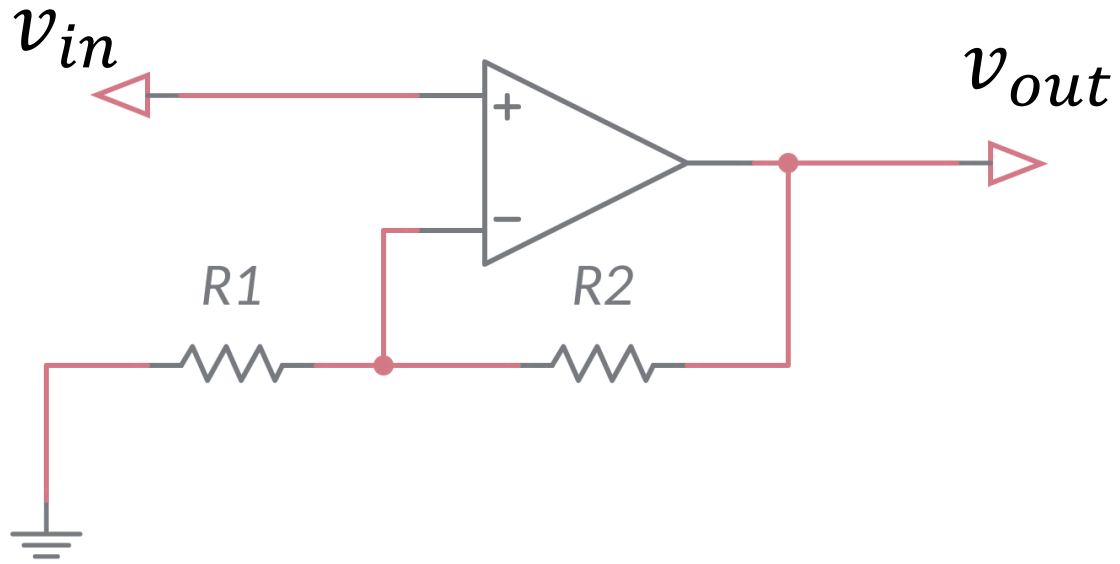


# Voltage follower

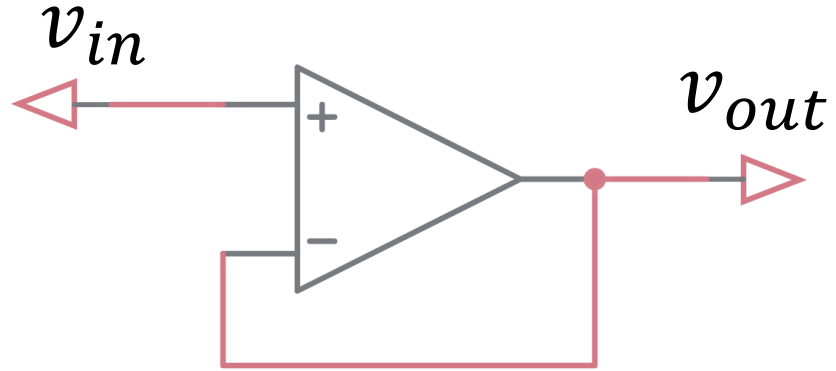

# Inverting Amplifier

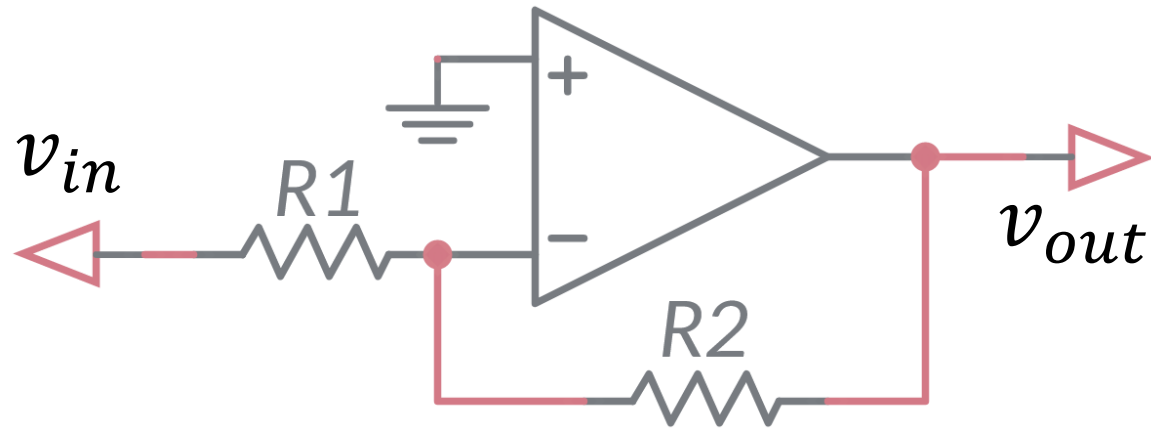


# Three OpAmp Instrumentation Amplifier

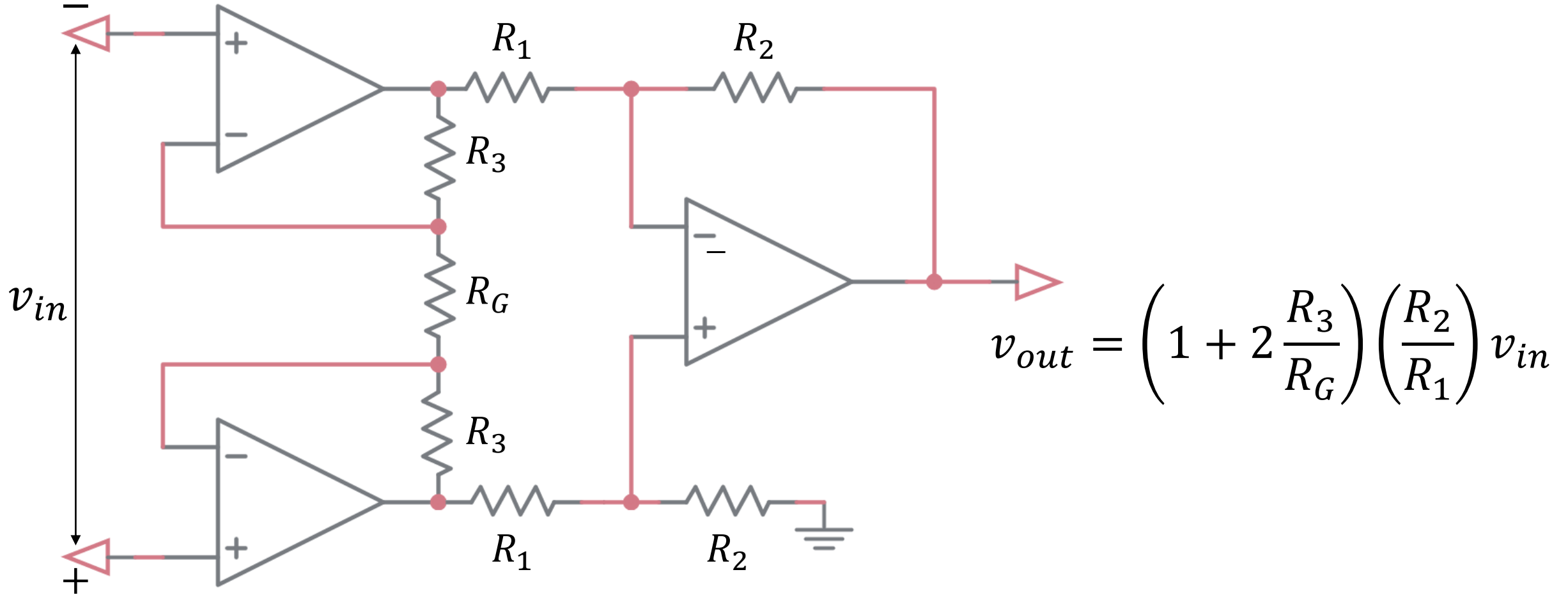


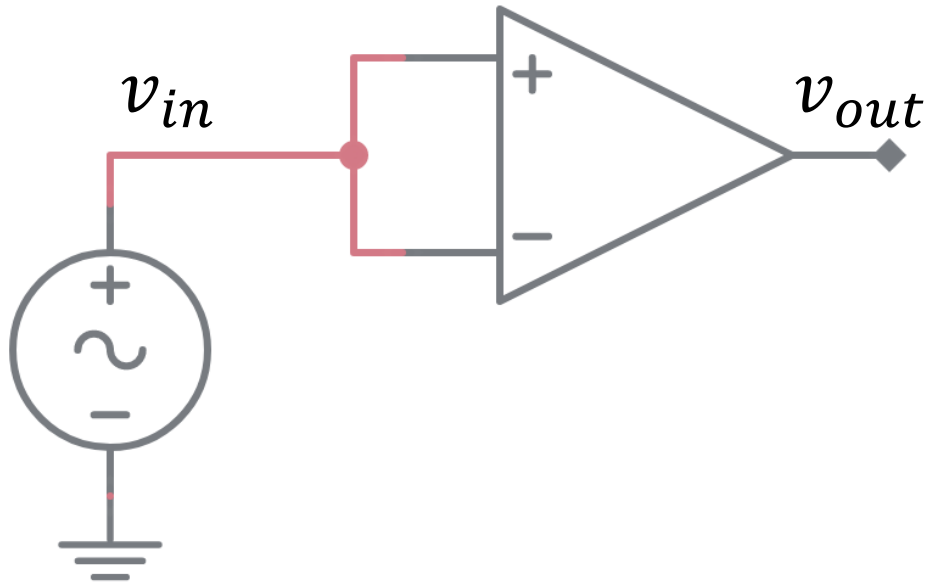
# Common Mode Rejection


- The ability of an op-amp to reject a common signal that appears at both its input terminals.







$$CMRR = 20 \log_{10} \left( \frac{g}{v_{out}/v_{in}} \right)$$
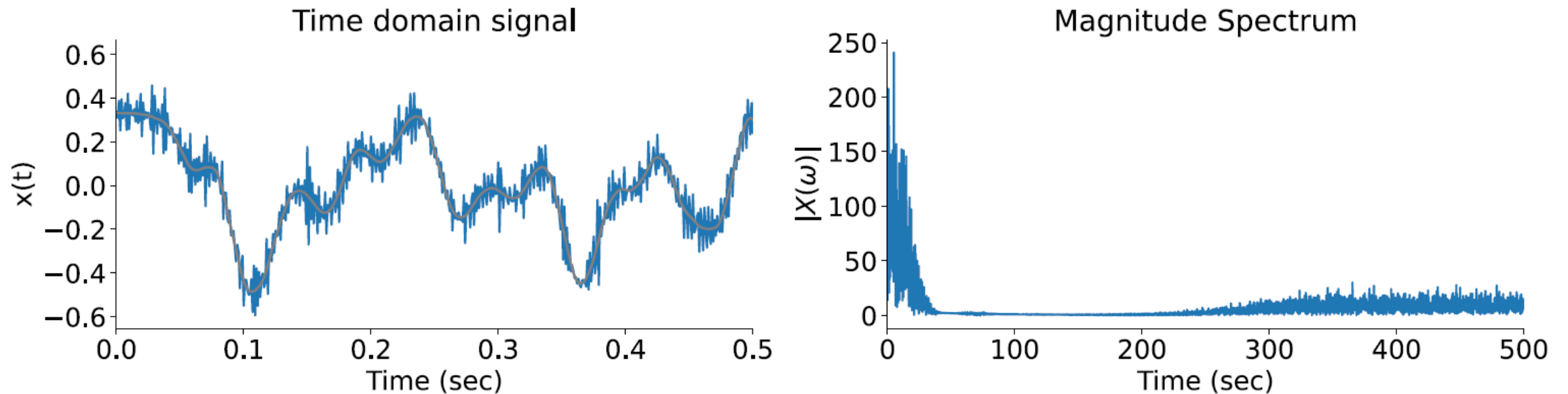
# Frequency selective filters

- LTI system can be used for implementing frequency selective filters, i.e. to modify the amplitude and phase of sinusoidal signals without affecting their frequency.





# Frequency selective filters

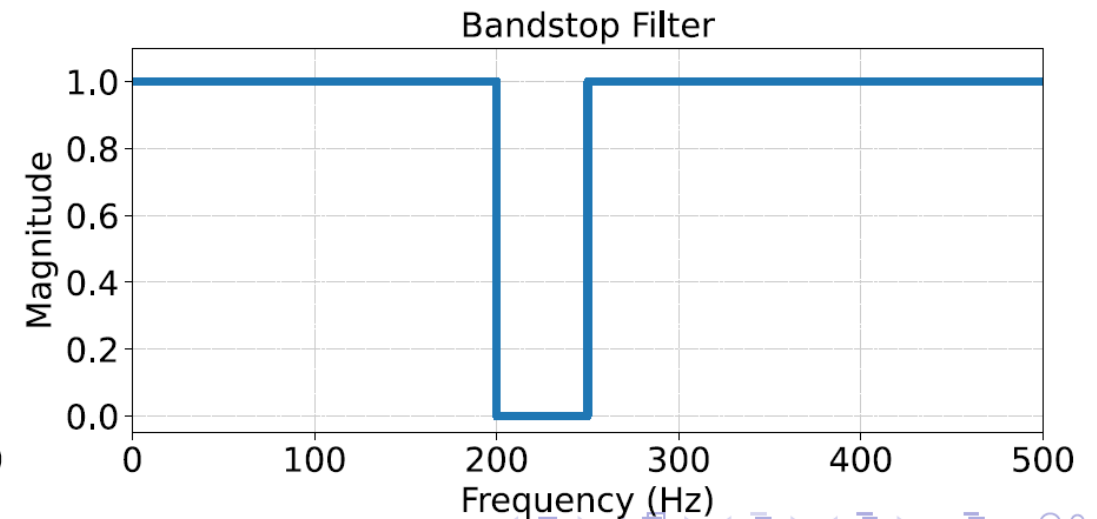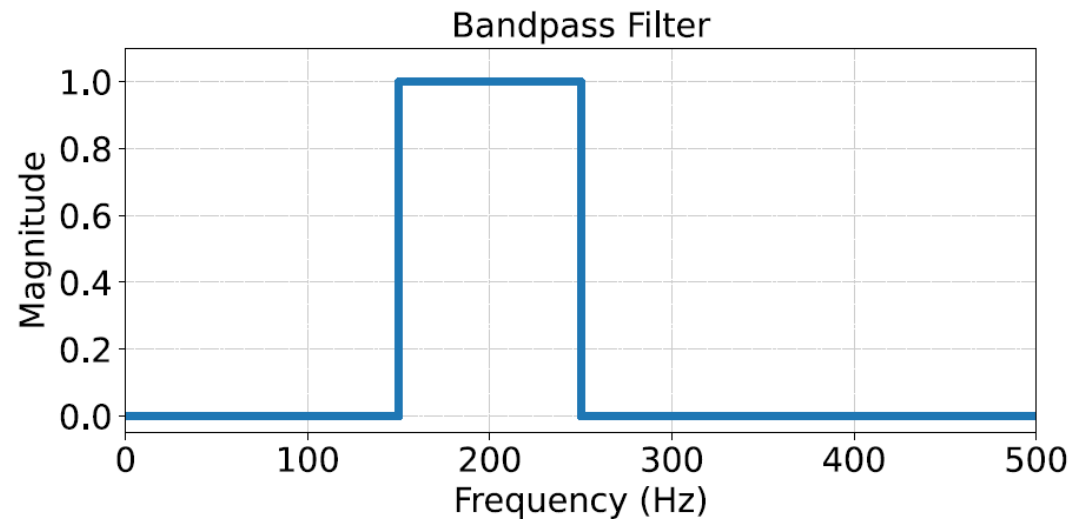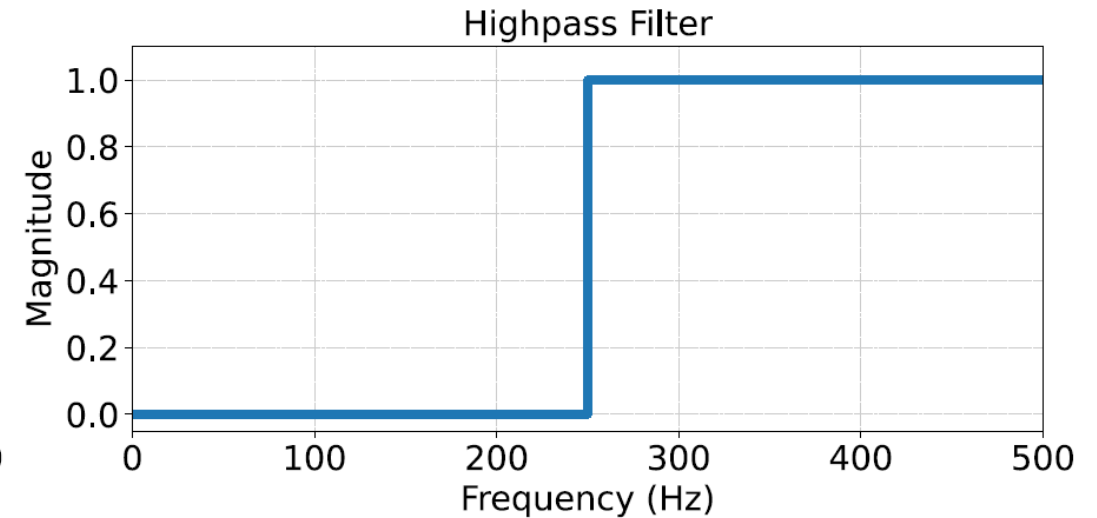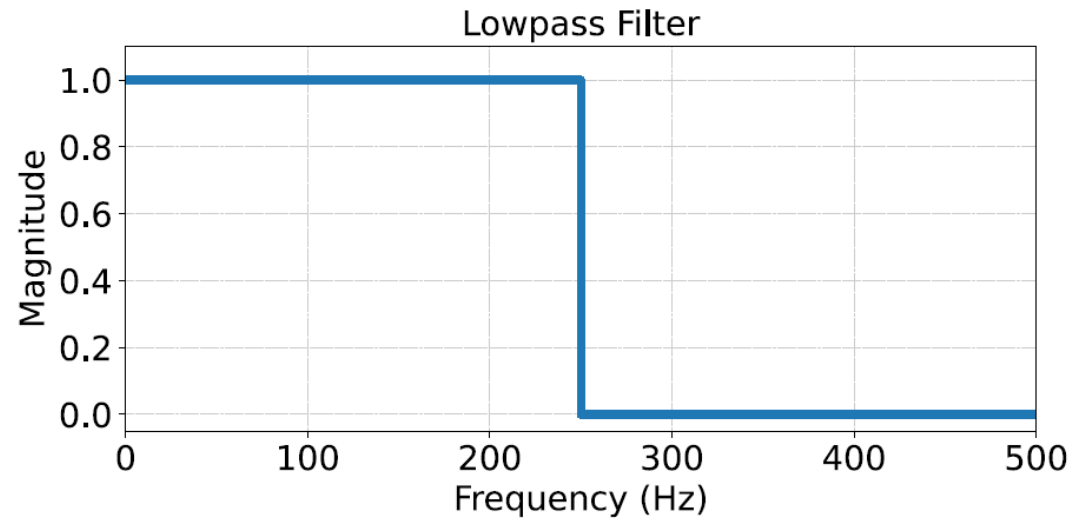
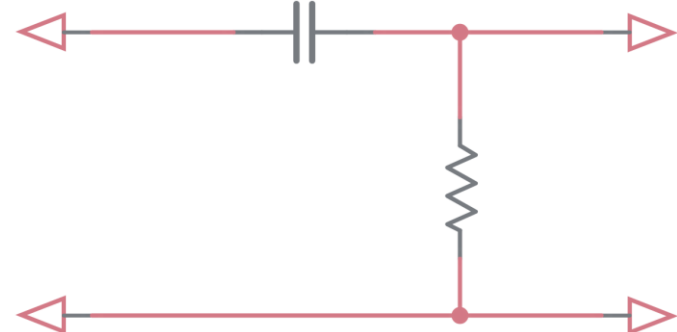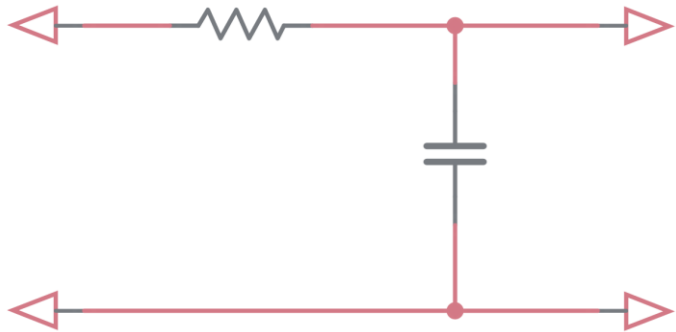
# Passive filters


- Passive filters are made from passive elements – resistors, capacitors, and inductors.



# Active filters

- Active filter use active elements, e.g. op-amp.
  - Avoid attenuation introduced by the filter in the passband.
  - Provide interstage isolations.
  - Can implement filters without inductors.



# Active Lowpass Filter

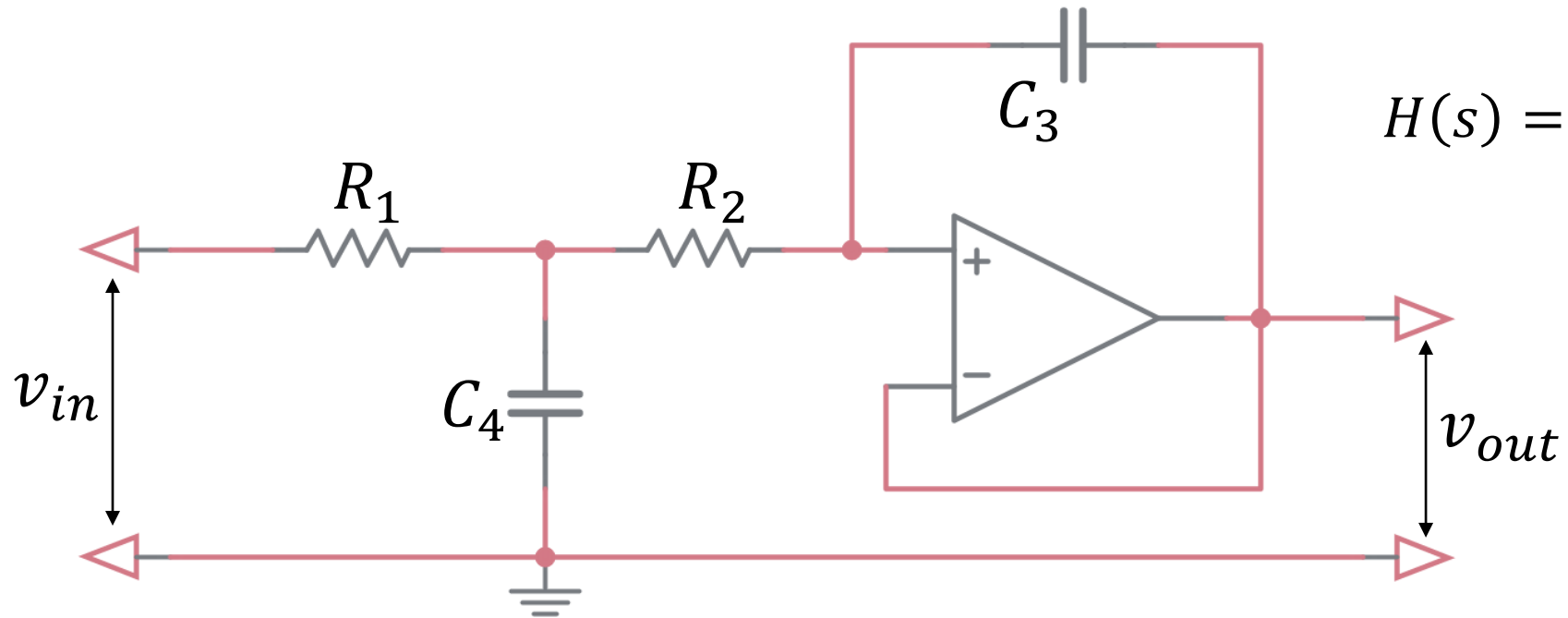


$$H(s) = \frac{Z_3 Z_4}{Z_1 Z_2 + Z_3 (Z_1 + Z_2) + Z_3 Z_4}$$

$$\begin{aligned} Z_1 &= R_1 \\ Z_2 &= R_2 \\ Z_3 &= \frac{1}{sC_3} \\ Z_4 &= \frac{1}{sC_4} \end{aligned}$$
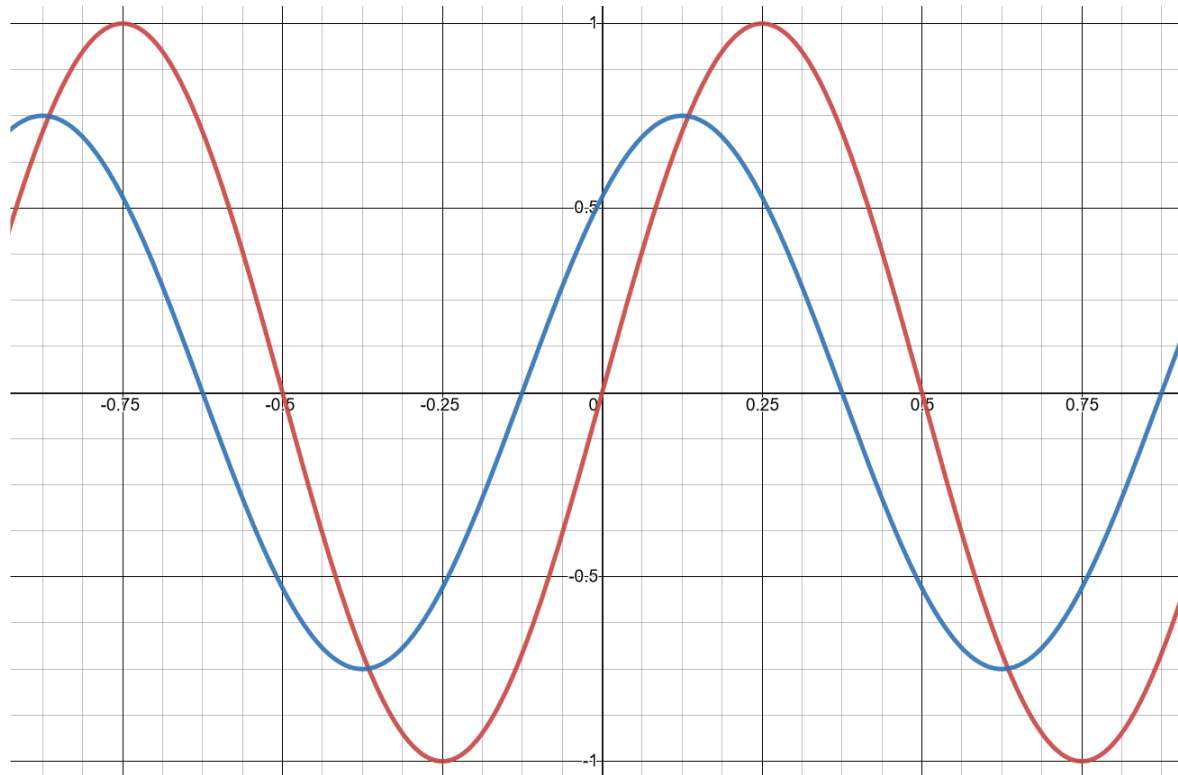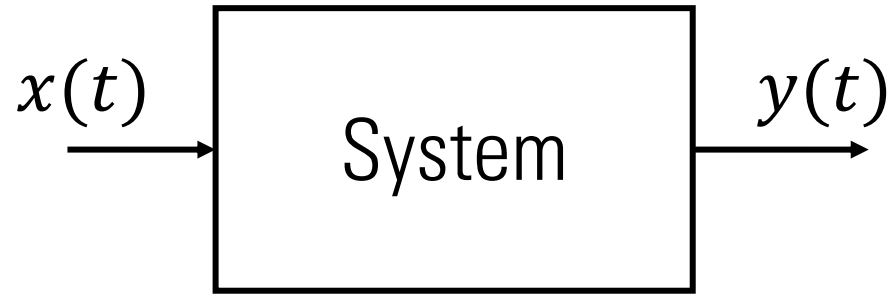
# Determining the frequency response of a system


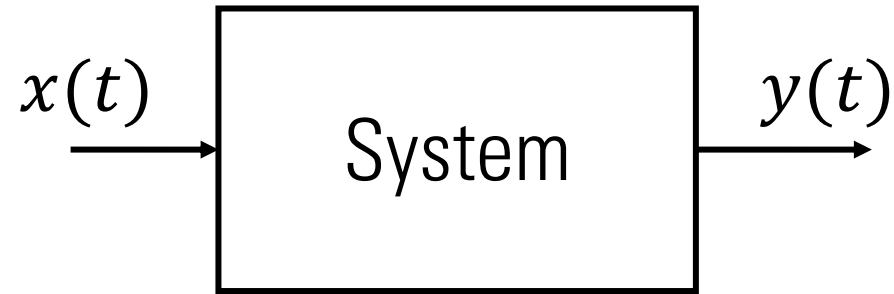
# Determining the frequency response of a system



$$H(j\omega) = \frac{Y(j\omega)}{X(j\omega)}$$